



# **Circuit and System Design**

## Part 2: Digital Systems




**FAKULTÄT ELEKTROTECHNIK  
UND INFORMATIONSTECHNIK**


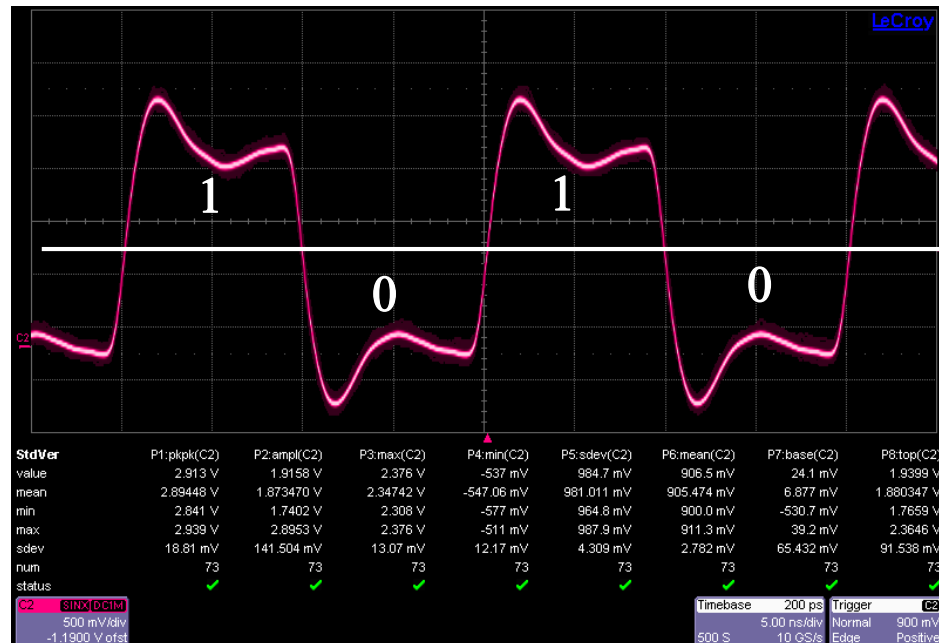
# Logic Circuits

- 2-valued representation:
  - 0, LOW, L, FALSE
  - 1, HIGH, H, TRUE
- Electrical representation as voltage signal:
  - $V_{\text{sig}} > V_{\text{th}} \rightarrow 1$
  - $V_{\text{sig}} < V_{\text{th}} \rightarrow 0$



- Connecting (relating) input variables to output variables

$$\boxed{(Z_1, Z_2, \dots) = F(A_1, A_2, \dots)}$$

- Forms of representation:
  - Logic equations
  - Truth table
  - Gate netlist

- Operators:

- Inversion:

$$Z = \bar{A}$$

A	Z
0	1
1	0

- AND:

$$Z = A_1 \cdot A_2$$

A <sub>1</sub>	A <sub>2</sub>	Z
0	0	0
0	1	0
1	0	0
1	1	1

- OR:

$$Z = A_1 + A_2$$

A <sub>1</sub>	A <sub>2</sub>	Z
0	0	0
0	1	1
1	0	1
1	1	1

- Calculation rules:

	Operation + (OR)	Operation · (AND)
1)	$(x + y) + z = x + (y + z)$	$(xy)z = x(yz)$
2)	$(x + y) = (y + x)$	$(xy) = (yx)$
3)	$x + xy = x$	$x(x + y) = x$
4)	$x + yz = (x + y)(x + z)$	$x(y + z) = xy + xz$
5)	$x + \bar{x} = 1$	$x\bar{x} = 0$
6)	$x + 0 = x$	$x1 = x$
7)	$x + 1 = 1$	$x0 = 0$
8)	$x + x = x$	$xx = x$
8)	$\overline{x + y} = \bar{x}\bar{y}$	$\overline{xy} = \bar{x} + \bar{y}$
9)	$\bar{\bar{x}} = x$	

- Representation of a logic function as a table

inputs			outputs	
$A_1$	$A_2$	$A_3$	$Z_1$	$Z_2$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	0
1	1	1	0	0

- Reduction of truth tables by Don't care (**X**)
- → Values which have no effect on the outputs

inputs			outputs	
A <sub>1</sub>	A <sub>2</sub>	A <sub>3</sub>	Z <sub>1</sub>	Z <sub>2</sub>
X	0	0	0	0
X	0	1	1	1
X	1	0	1	0
X	1	1	0	0



- Relation between Min- or Max-terms of a logic function
- **Minterm:**
  - For exactly one output assignment of inputs = 1
  - OR function to connect minterms to get output value

inputs			outputs	
A <sub>1</sub>	A <sub>2</sub>	A <sub>3</sub>	Z <sub>1</sub>	Z <sub>2</sub>
X	0	0	0	0
X	0	1	1	1
X	1	0	1	0
X	1	1	0	0

Minterms

$$Z_1 = \overline{A_2} \cdot A_3 + A_2 \cdot \overline{A_3}$$

$$Z_2 = \overline{A_2} \cdot A_3$$

- **Maxterm:**

- For exactly one output assignment of inputs = 0
- AND function to connect maxterms to get output value

inputs			outputs	
$A_1$	$A_2$	$A_3$	$Z_1$	$Z_2$
X	0	0	0	0
X	0	1	1	1
X	1	0	1	0
X	1	1	0	0

Maxterms

$$Z_1 = (A_2 + A_3) \cdot (\overline{A_2} + \overline{A_3})$$

$$Z_2 = (A_2 + A_3) \cdot (\overline{A_2} + A_3) \cdot (\overline{A_2} + \overline{A_3})$$

- A method for simplifying logic functions
- Modified arrangement of the truth table values
- Karnaugh map with

- 2 inputs:

z	$A_1$	$\overline{A_1}$
$A_2$		
$\overline{A_2}$		

- 3 inputs:

z	$A_1A_2$	$\overline{A_1}A_2$	$\overline{A_1}\overline{A_2}$	$A_1\overline{A_2}$
$A_3$				
$\overline{A_3}$				

- 4 inputs:

z	$A_1A_2$	$\overline{A_1}A_2$	$\overline{A_1}\overline{A_2}$	$A_1\overline{A_2}$
$A_3A_4$				
$\overline{A_3}A_4$				
$\overline{A_3}\overline{A_4}$				
$A_3\overline{A_4}$				

- Enter the values in logic table into Karnaugh map
- **Minterm** method:
  - Bringing together the fields, which contain 1 (miniterms)
  - Converting these fields into connected terms (AND functions)
  - Omitting variables in negated and not negated form
  - ORing these terms

Z	$A_1A_2$	$\overline{A_1}A_2$	$\overline{A_1}\overline{A_2}$	$A_1\overline{A_2}$
$A_3A_4$	1	1	0	0
$\overline{A_3}A_4$	0	0	1	1
$\overline{A_3}\overline{A_4}$	0	0	1	1
$A_3\overline{A_4}$	1	1	0	0

$$Z = \overline{A_2} \cdot \overline{A_3} + A_2 \cdot A_3$$

- **Maxterm** method:
  - Bringing together the fields, which contain 0 (maxterms)
  - Converting these fields into connected terms (OR functions), Inversion of variables
  - Omitting variables in negated and not negated form
  - ANDing these terms

Z	$A_1A_2$	$\overline{A_1}A_2$	$\overline{A_1}\overline{A_2}$	$A_1\overline{A_2}$
$A_3A_4$	1	1	0	0
$\overline{A_3}A_4$	0	0	1	1
$\overline{A_3}\overline{A_4}$	0	0	1	1
$A_3\overline{A_4}$	1	1	0	0

$$Z = (\overline{A_2} + \overline{A_3}) \cdot (\overline{\overline{A_2}} + \overline{\overline{A_3}})$$

$$Z = (\overline{A_2} + A_3) \cdot (A_2 + \overline{A_3})$$


$$Z = \overline{A_2} \cdot \overline{A_3} + A_2 \cdot A_3$$

- Implementing logic functions using logic cells (Gates)
- Examples:


$$\text{INV: } Z = \bar{A}$$




$$\text{BUF: } Z = A$$

 


$$\text{AND2: } Z = A_1 \cdot A_2$$

 

$$\text{OR2: } Z = A_1 + A_2$$

 
 
$$\text{NAND2: } Z = \overline{A_1 \cdot A_2}$$





$$\text{NOR2: } Z = \overline{A_1 + A_2}$$



- Logic cell libraries additionally contain complex gates with >2 inputs
  - Adder, Multiplexer, AOI, OAI

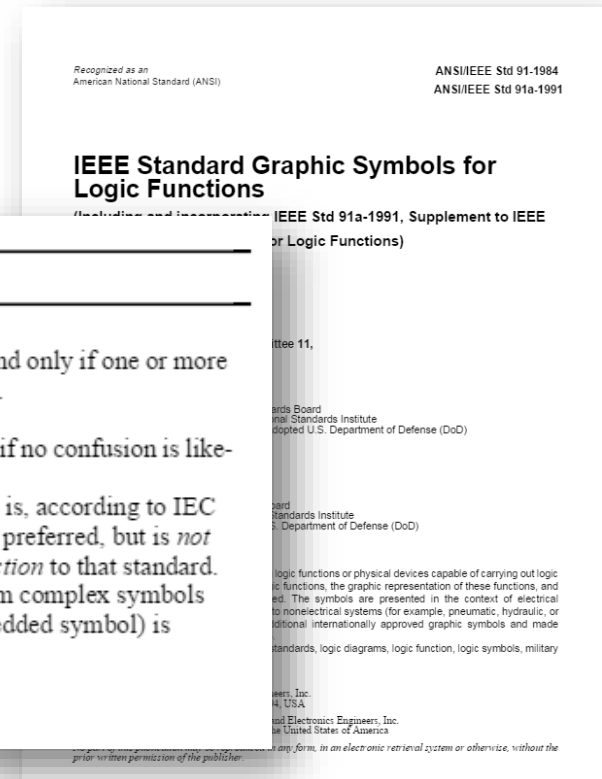
- Standardized representation of logic symbols
  - IEC 60617-12 : 1997
  - ANSI/IEEE Std 91/91a-1991



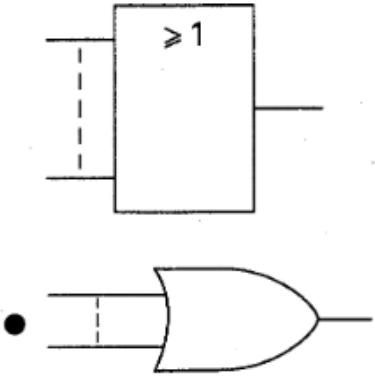No	Symbol	Description
5.1-1		<p>OR element, general symbol The output stands at its 1-state if and only if one or more of the inputs stand at their 1-states.</p> <p>NOTES:</p> <p>1 — “<math>\geq 1</math>” may be replaced by “1” if no confusion is likely.</p> <p>2 — The distinctive-shape symbol is, according to IEC Publication 617, Part 12, not preferred, but is <i>not considered to be in contradiction</i> to that standard. Its use in combination to form complex symbols (for example, use as an embedded symbol) is discouraged.</p>

- Widespread use of "distinctive-shape symbols" in manuals, standard cell libraries, scientific publications
- "... in the English-speaking world the American symbols (middle column) were and are common. *The IEC symbols have met with limited international acceptance and are (almost) consistently ignored in American literature.*" [https://en.wikipedia.org/wiki/Logic\\_gate](https://en.wikipedia.org/wiki/Logic_gate) (23.10.2015)

 
- Representation of logic function using gate circuits



- Representation of the logic function depending on the available gate
- Circuit Synthesis, Mapping



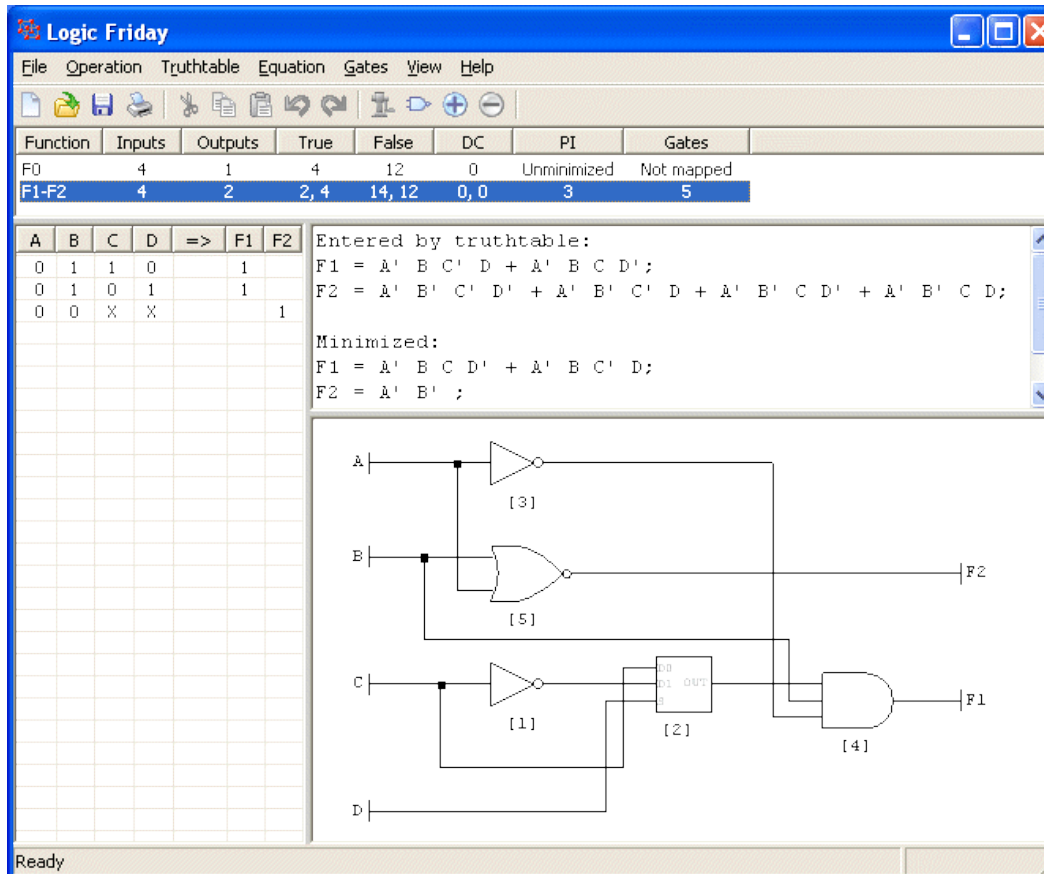- Freeware Logic Friday → [www.sontrak.com](http://www.sontrak.com)
- Representation, simplification and optimization of logic functions (equation, table, gate netlist)



**Logic Friday**

File Operation Truthtable Equation Gates View Help

Function	Inputs	Outputs	True	False	DC	PI	Gates
F0	4	1	4	12	0	Unminimized	Not mapped
F1-F2	4	2	2, 4	14, 12	0, 0	3	5

A	B	C	D	=>	F1	F2
0	1	1	0		1	
0	1	0	1		1	
0	0	X	X			1


Entered by truthtable:  
 $F1 = A' B C' D + A' B C D'$ ;  
 $F2 = A' B' C' D' + A' B' C' D + A' B' C D' + A' B' C D$ ;

Minimized:  
 $F1 = A' B C D' + A' B C' D$ ;  
 $F2 = A' B'$ ;

Logic Circuit Diagram:  
 Inputs: A, B, C, D  
 Outputs: F1, F2  
 Components:  
 [3] NOT gate (A)  
 [5] OR gate (B, C)  
 [1] NOT gate (C)  
 [2] 4-input AND gate (A, B, C, D)  
 [4] 3-input AND gate (A, B, C)  
 F2 is connected to the output of gate [5].  
 F1 is connected to the output of gate [4].


Ready

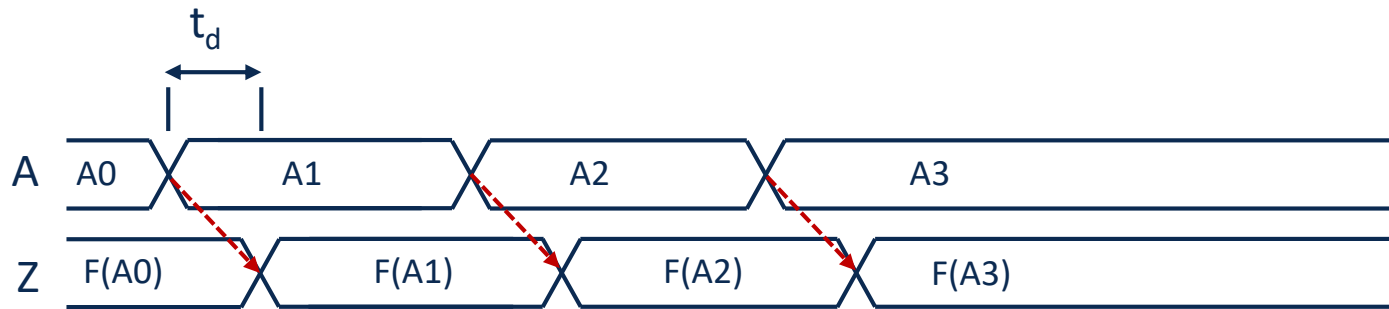- The output value changes **when** the input values **change** after a delay time  $t_d$  (Delay)
- The ideal delay time is  $t_d=0$
- Signal paths in circuits with multiple inputs and outputs may have different individual delays.




- Combinational circuits **do not include clocked memories**
- $Z = F(A)$

- $Z = F(A)?$

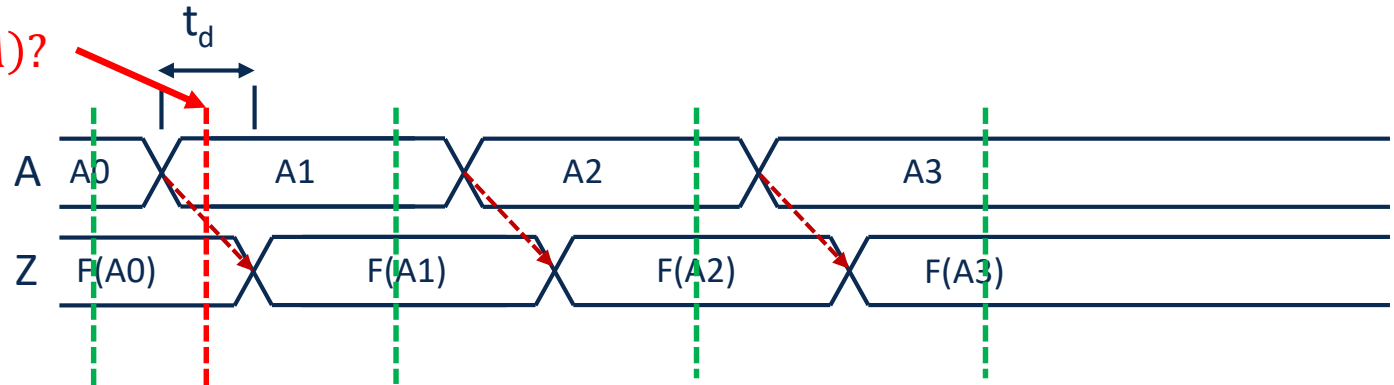


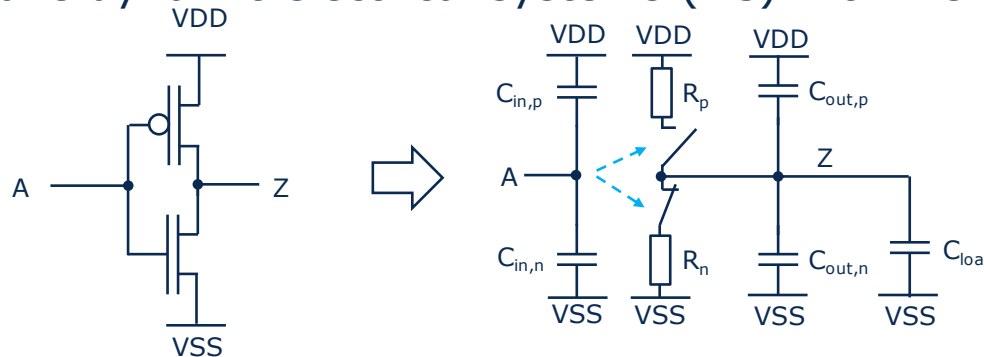- Combinational circuits **do not include clocked memories**
- **BUT:** They have dynamic electrical systems (RC) with memory





- → Observing signals at **defined times** when  $Z = F(A)$
- → Application of combinational logic theory **without memory.**

 - Sequential logic circuits **include clocked memory**
- Memory state  $S$
- Considering the system at times  $(i, i+1, i+2, \dots)$ , e.g. realised by a clocked signal (clock)




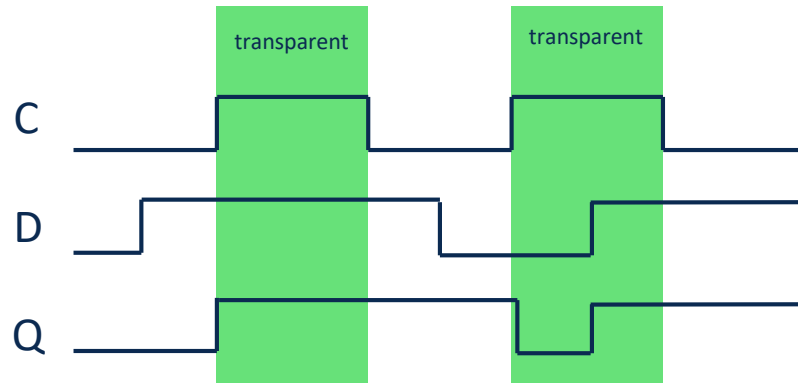 - Level-triggered storage element
- Inputs:
  - D: Data input
  - C: Clock (alternatively also E: Enable)
    - C=1 turns the latch transparent (Memory is written)
- Output:
  - Q: Data Output




D	C	Q
0	1	0
1	1	1
X	0	$Q_{i-1}$

 - Interrupting the clock signal by a control signal EN (enable)  $EN=0 \rightarrow CEN=0$
- Reduction of power consumption of temporarily unused circuit parts





## Solution A


 


Glitch




## Solution B

  

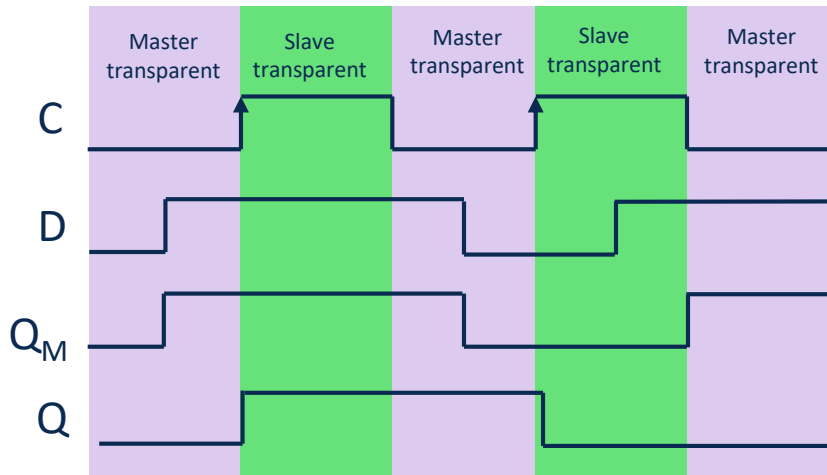
 


D	C	Q
0	↑	0
1	↑	1
X	↓	Q <sub>i-1</sub>



- Additional asynchronous input for defining an initial state **independent of Clock C**
- Possible with latches and flipflops
- Only active to one logic level (active-high (1), active low (0))
  - Active-high Set S: active when  $S=1$  →  $Q_0 = 1$
  - Active-low Set SN: active when  $SN=0$  →  $Q_0 = 1$
  - Active-high Reset R: active when  $R=1$  →  $Q_0 = 0$
  - Active-low Reset RN: active when  $RN=0$  →  $Q_0 = 0$




 




  

RN	D	C	Q
1	0	↑	0
1	1	↑	1
1	X	↓	$Q_{i-1}$
0	X	X	0

  


 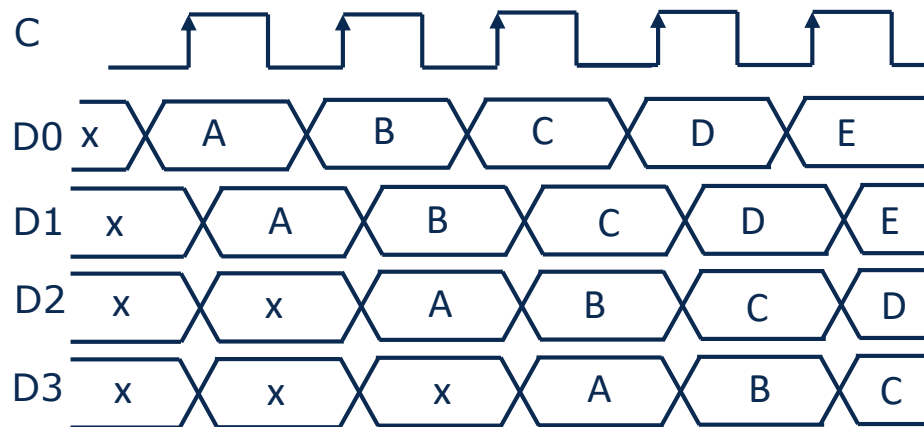  

- Finite-State Machines (FSM) are the basic components of digital control units
- FSMs are sequential digital systems


- **Mealy Machine**

 - $S_{i+1} = G(A_i, S_i)$
- $Z_i = F(A_i, S_i)$





- **Moore Machine**

 
- $S_{i+1} = G(A_i, S_i)$
- $Z_i = F(S_i)$





  - Representation of states and their transitions
- Unique label for each state
- Marking of the **Reset** state



- Assignment of a unique binary word for each state
  - With  $m$  states  $\rightarrow$   $N$  state bits with  $2^N \geq m$
  - Coding of the  $2^N - m$  unused states as well!
- State coding affects:
  - Power consumption
    - $\rightarrow$  Reduction of signal changes in the state word for the most frequently expected routes through the state graph
  - Complexity of state transition logic and output logic
- Example:
  - **Binary-Code**  $\rightarrow$  6 Toggles in **S** per flow
  - **Gray-Code**  $\rightarrow$  4 Toggles in **S** per flow

 

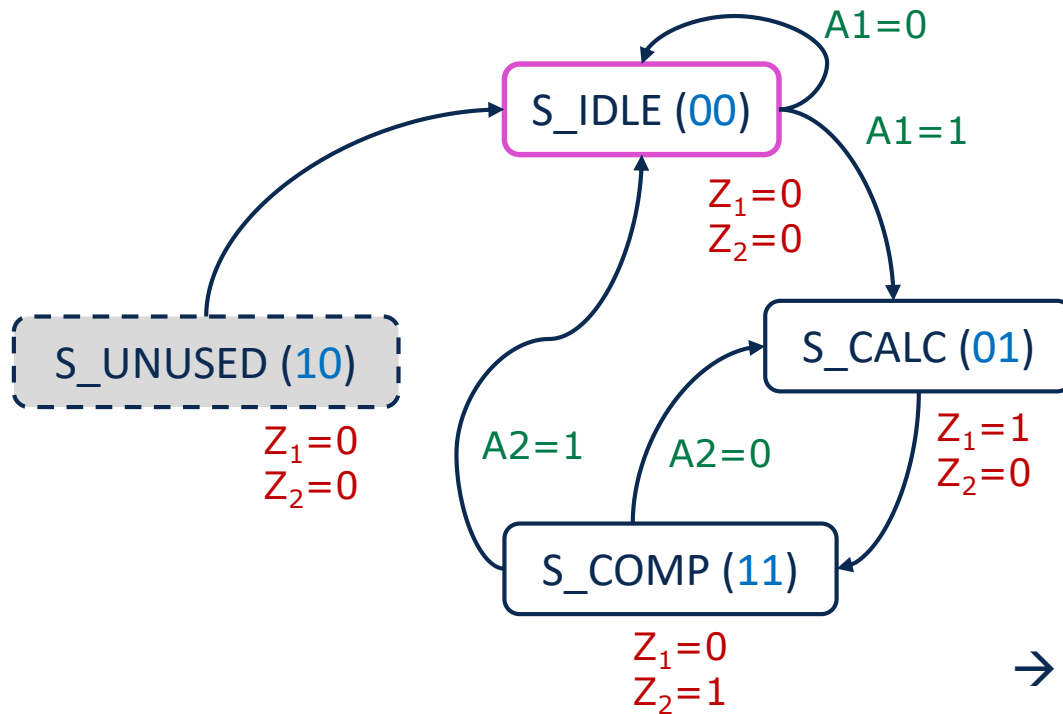 

→ 2-Bit state variable

$S_{1,i}$	$S_{0,i}$	$A_2$	$A_1$	$S_{1,i+1}$	$S_{0,i+1}$
0	0	x	0	0	0
0	0	x	1	0	1
0	1	x	x	1	1
1	0	x	x	0	0
1	1	0	x	0	1
1	1	1	x	0	0

$S_{1,i}$	$S_{0,i}$	$Z_{2,i}$	$Z_{1,i}$
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	0






$S_{1,i+1}$	$S_1 S_0$	$\bar{S}_1 S_0$	$\bar{S}_1 \bar{S}_0$	$S_1 \bar{S}_0$
$A_1 A_2$	0	1	0	0
$\bar{A}_1 A_2$	0	1	0	0
$\overline{A_1 A_2}$	0	1	0	0
$A_1 \bar{A}_2$	0	1	0	0

$S_{0,i+1}$	$S_1 S_0$	$\bar{S}_1 S_0$	$\bar{S}_1 \bar{S}_0$	$S_1 \bar{S}_0$
$A_1 A_2$	0	1	1	0
$\bar{A}_1 A_2$	0	1	0	0
$\overline{A_1 A_2}$	1	1	0	0
$A_1 \bar{A}_2$	1	1	1	0

$$S_{1,i+1} = \bar{S}_1 S_0$$
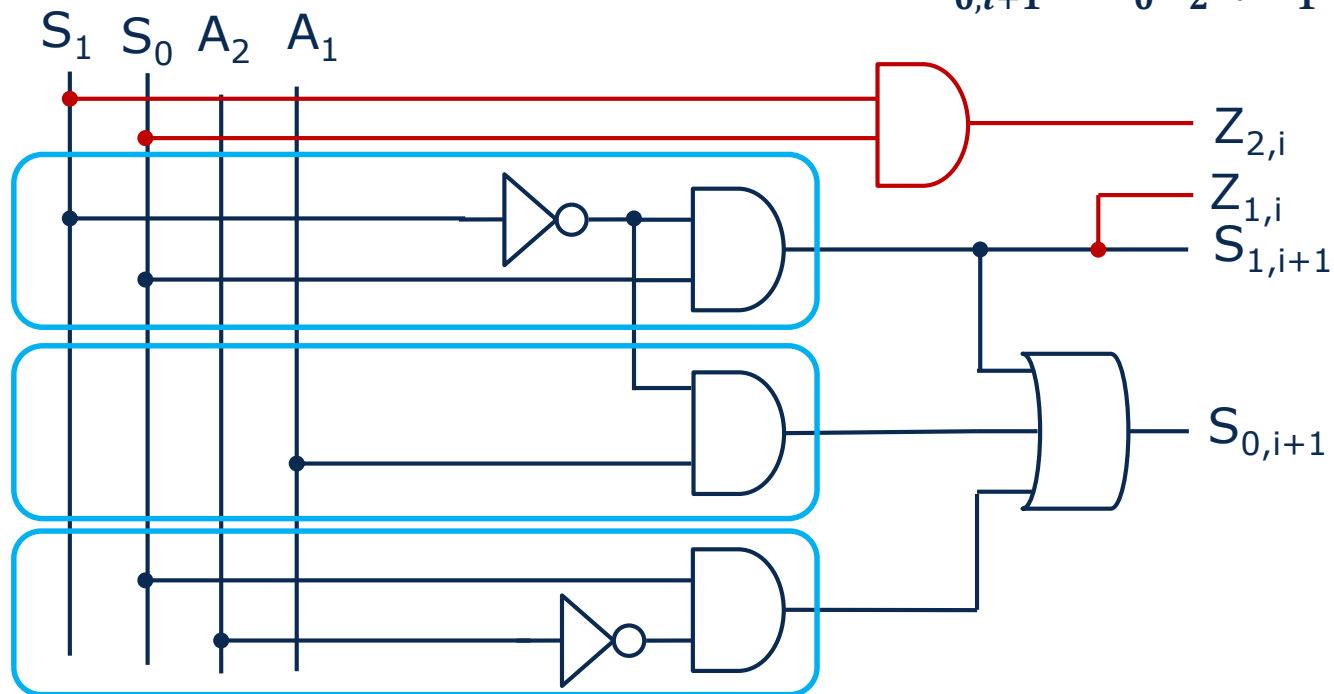
$$S_{0,i+1} = S_0 \bar{A}_2 + \bar{S}_1 S_0 + \bar{S}_1 A_1$$



 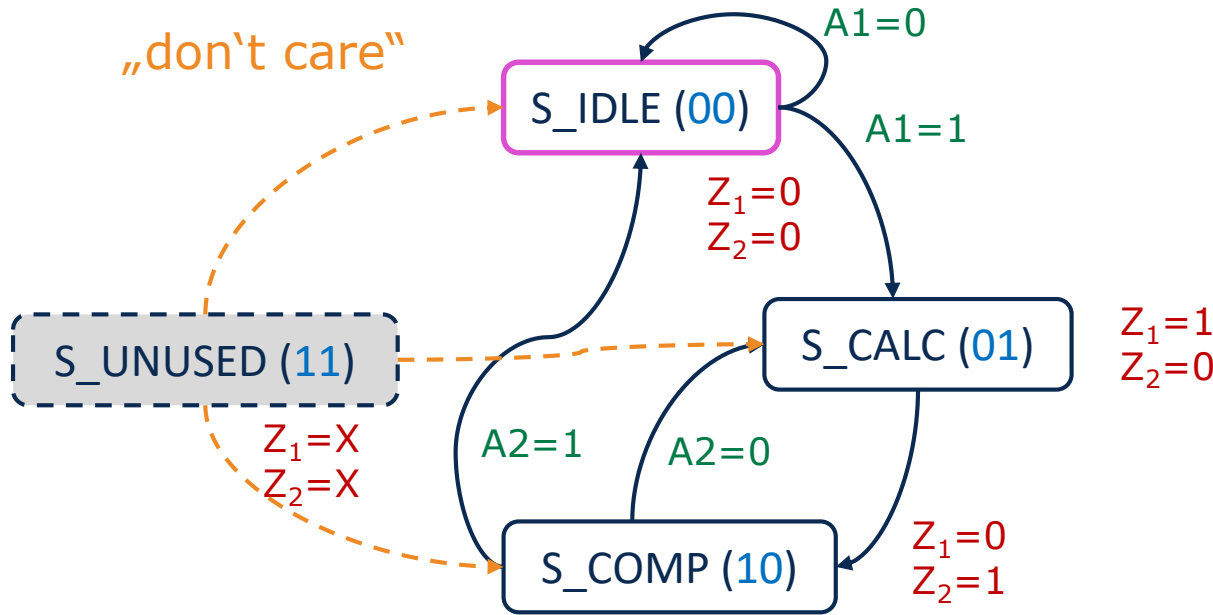

$S_{1,i}$	$S_{0,i}$	$A_2$	$A_1$	$S_{1,i+1}$	$S_{0,i+1}$
0	0	X	0	0	0
0	0	X	1	0	1
0	1	X	X	1	0
1	0	0	X	0	1
1	0	1	X	0	0
1	1	X	X	X	X


$S_{1,i}$	$S_{0,i}$	$Z_{2,i}$	$Z_{1,i}$
0	0	0	0
0	1	0	1
1	0	1	0
1	1	X	X

$S_{1,i+1}$	$S_1 S_0$	$\bar{S}_1 S_0$	$\bar{S}_1 \bar{S}_0$	$S_1 \bar{S}_0$
$A_1 A_2$	X	1	0	0
$\bar{A}_1 A_2$	X	1	0	0
$\bar{A}_1 \bar{A}_2$	X	1	0	0
$A_1 \bar{A}_2$	X	1	0	0

$S_{0,i+1}$	$S_1 S_0$	$\bar{S}_1 S_0$	$\bar{S}_1 \bar{S}_0$	$S_1 \bar{S}_0$
$A_1 A_2$	X	0	1	0
$\bar{A}_1 A_2$	X	0	0	0
$\bar{A}_1 \bar{A}_2$	X	0	0	1
$A_1 \bar{A}_2$	X	0	1	1

$$S_{1,i+1} = S_0$$
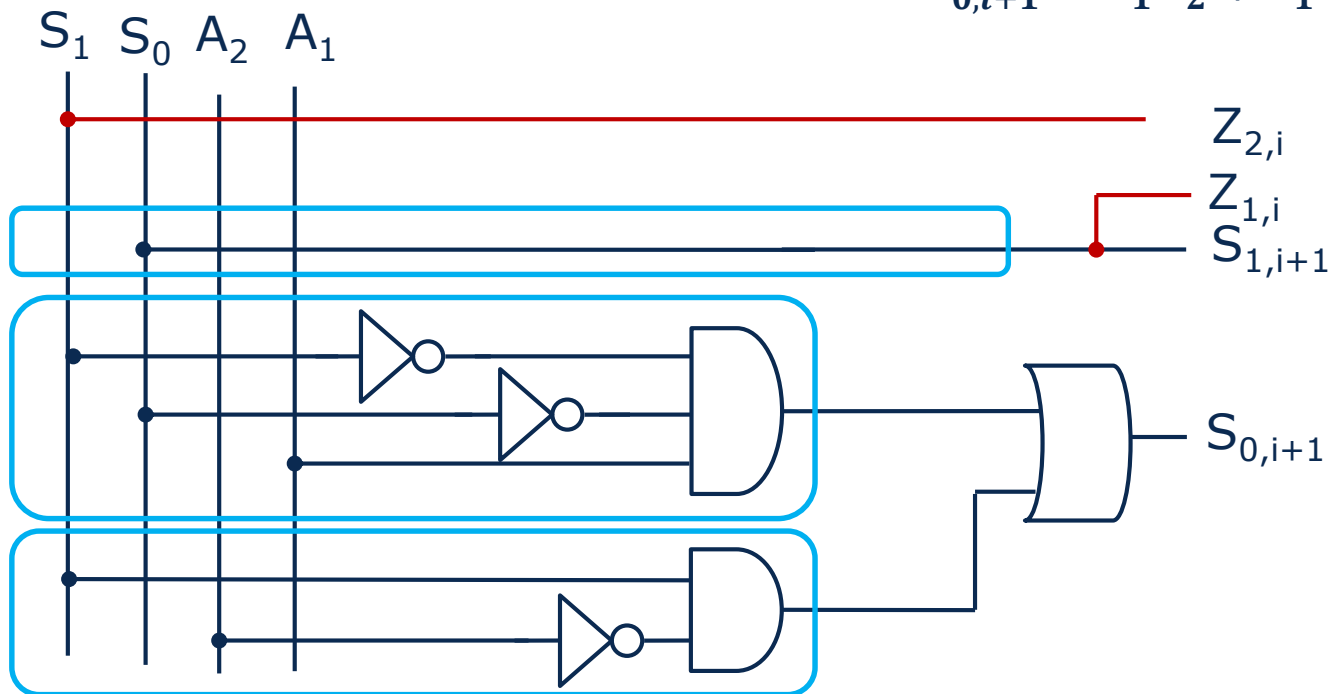
$$S_{0,i+1} = S_1 \bar{A}_2 + \bar{S}_1 \bar{S}_0 A_1$$



23.10.2019

1. Set up state-transition diagram
2. Determine the number of state bits and state coding
3. State-transition table and output table
4. Simplification of logic (Karnaugh, equation)
5. Create a gate netlist


# Arithmetic - Number Formats

- Representation of unsigned integers as n-bit vector

- $b \in (0; 1)$

- Decimal value: 
$$D = \sum_{i=0}^{n-1} b_i \cdot 2^i$$

- Value range:  $0 \leq D \leq 2^n - 1$

 

„most significant bit“ (MSB)

„least significant bit“ (LSB)

Decimal	Binary	Hexadecimal
0	0b0000	0x0
1	0b0001	0x1
2	0b0010	0x2
3	0b0011	0x3
4	0b0100	0x4
5	0b0101	0x5
6	0b0110	0x6
7	0b0111	0x7
8	0b1000	0x8
9	0b1001	0x9
10	0b1010	0xA
11	0b1011	0xB
12	0b1100	0xC
13	0b1101	0xD
14	0b1110	0xE
15	0b1111	0xF

- 1-bit Addition  $a+b$

a	b	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Example Addition:

$$\begin{array}{r}
 \phantom{+} \phantom{Carry} \phantom{Sum} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{(5)} \\
 \phantom{+} \phantom{Carry} \phantom{Sum} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{(5)} \\
 + \phantom{Carry} \phantom{Sum} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{(5)} \\
 \hline
 \text{Carry} \phantom{Sum} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{(5)} \phantom{1} \\
 \phantom{Carry} \text{Sum} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{(5)} \phantom{1} \\
 \phantom{Carry} \phantom{Sum} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{(5)} \phantom{1} \phantom{0} \phantom{0} \phantom{1} \phantom{0} \phantom{(2)}
 \end{array}$$

- Addition of  $n$ -bit numbers  $\rightarrow n+1$  bit output



- 1-bit Multiplication  $a \cdot b$


a	b	$a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

- Example:  $0b1001 \cdot 0b0101$  (9·5)

				1	0	0	1		
				1	0	0	1		1
+			0	0	0	0			0
+		1	0	0	1				1
+	0	0	0	0					0
Product	0	0	1	0	1	1	0	1	(45)

- Multiplication of  $n$ -bit numbers  $\rightarrow$   $2n$ -bit output

 - Representation of signed integer numbers as n-bit vector
- $b \in (0; 1)$
- 2's complement representation
- Decimal value:
  - positive number: when  $b_{n-1}=0$ :  $D = \sum_{i=0}^{n-1} b_i \cdot 2^i$
  - negative number: when  $b_{n-1}=1$ :  $D = -1 \cdot (\sum_{i=0}^{n-1} \bar{b}_i \cdot 2^i + 1)$
- Value range:  $-2^{n-1} \leq D \leq 2^{n-1} - 1$



„sign bit“

„least significant bit“ (LSB)

Decimal value	Binary Signed (2's complement)
0	0b0000
1	0b0001
2	0b0010
3	0b0011
4	0b0100
5	0b0101
6	0b0110
7	0b0111
-8	0b1000
-7	0b1001
-6	0b1010
-5	0b1011
-4	0b1100
-3	0b1101
-2	0b1110
-1	0b1111

- calculation of  $-1 \cdot A$ 
  1. Inversion of all bits of A
  2. Addition of +1
- Example:
  - $-1 \cdot 3 = -1 \cdot (0b0011) \rightarrow 0b1100 + 0b0001 = 0b1101 = -3$
  - $-1 \cdot (-3) = -1 \cdot (0b1101) \rightarrow 0b0010 + 0b0001 = 0b0011 = 3$

- Example 1:

		0	0	1	0	(2)
	+	1	1	1	0	(-2)
Carry		1	1	1	0	
Sum		0	0	0	0	(0)

OK

- Example 2:

		1	1	1	0	(-2)
	+	1	1	1	0	(-2)
Carry		1	1	1	0	
Sum		1	1	0	0	(-4)

OK

- Example 3:

		0	1	0	0	(4)
	+	0	1	1	0	(6)
Carry		0	1	0	0	
Sum		1	0	1	0	(-6)

**Error**  
Addition of pos.  
numbers must  
give pos. result!

- Example 4:

		1	1	0	0	(-4)
	+	1	0	1	0	(-6)
Carry		1	0	0	0	
Sum		0	1	1	0	(6)


**Error**  
Addition of neg.  
numbers must  
give neg. result!

- Carry: Carry out the highest binary digit (MSB) in the **unsigned** range
- Overflow: Detection of the **signed** range overflows

Sign(A)	Sign(B)	Sign(A+B)	Overflow
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Decimal value	Unsigned representation	Signed representation
Carry Bit	<b>Error</b>	not relevant
Overflow Bit	not relevant	<b>Error</b>

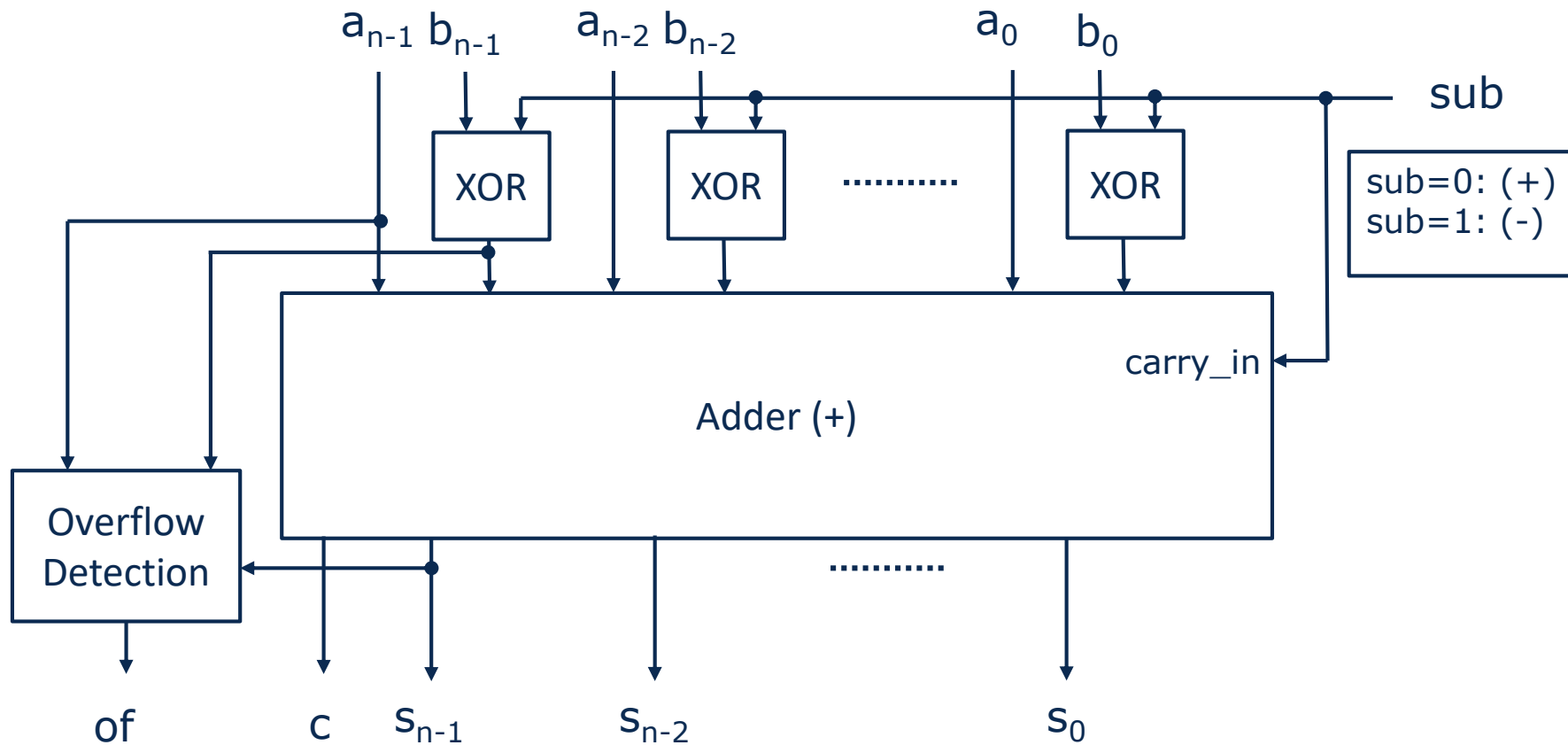
- Addition and Subtraction can be done with the same circuit



- Representation of numbers with decimal point and decimal places as n-bit vector
- k **decimal** und n-k **predecimal**
- Values of LBS:  $2^{-k}$

- Decimal value: 
$$D = \sum_{i=0}^{n-1} b_i \cdot 2^{i-k}$$

 - Value range:  $0 \leq D \leq (2^n - 1) \cdot 2^{-k}$



„most significant bit“ (MSB)

„Point“

„least significant bit“ (LSB)

Representation of signed fixed-point numbers analogous to integers (scaling with  $2^{-k}$ )



- Addition/Subtraction of n-bit Fixed-Point numbers:
  - $A = a \cdot 2^{-k}$ ,  $B = b \cdot 2^{-k} \rightarrow A \pm B = (a \pm b) \cdot 2^{-k}$
  - (n+1)-bit output

- Example 1:

- n=4, k=2,  $2^{-k}=0.25$ , unsigned

		0	1		1	0	(1.50)
	+	1	0		0	1	(2.25)
Carry		0	0		0		
Sum		1	1		1	1	(3.75)

- Example 2:


- n=4, k=2,  $2^{-k}=0.25$ , signed

		0	1		1	0	(1.50)
	+	1	0		1	1	(-1.25)
Carry		1	1		0		
Sum		0	0		0	1	(0.25)

- Multiplication of n-bit Fixed-Point numbers:
  - $A = a \cdot 2^{-k}$ ,  $B = b \cdot 2^{-k} \rightarrow A \cdot B = (a \cdot b) \cdot 2^{-2k}$
  - $\rightarrow$  Doubling the number of decimal places
  - 2n-Bit output with  $2^{-2k}$  LSB accuracy
- Example:
  - $n=4$ ,  $k=2$ ,  $2^{-k}=0.25$ , unsigned
  - $0b1001 \cdot 0b0101$  ( $2.25 \cdot 1.25$ )

				1	0	0	1	
				1	0	0	1	1
+			0	0	0	0		0
+		1	0	0	1			1
+	0	0	0	0				0
Product	0	0	1	0	1	1	0	1
								(2.8125)

 - Multiplication of  $n$ -bit values  $\rightarrow$   $2n$ -bit output
- For  $n$ -Bit data buses, scaling is necessary  $c = \text{Scale}(b)$



- In SSE lab exercise:
  - **SCALER64\_to\_32**: Determination of overflows (signed, unsigned)
  - Indication of the number  $k$  LSBs
  - Use only when overflow signals are needed
  - Otherwise: direct wiring of the bus signals


- Division of n-bit Fixed-Point numbers:
  - $A = a \cdot 2^{-k}$ ,  $B = b \cdot 2^{-k} \rightarrow A/B = (a/b) \cdot 2^{-k+k} = a/b$
- For n-bit operands:
  - n-bit integer result + n-bit **Remainder (Modulo)**
    - Example:  $0b1101 / 0b0011$  ( $13/3$ ) =  $0b0100$  Remainder:  $0b0001$
    - SSE lab : **DIV\_FIXED32\_signed** and **DIV\_FIXED32\_unsigned**
  - n-bit integer result + infinitely many decimal places
    - Example:  $0b1101 / 0b0011$  ( $13/3$ ) =  $0b0100,010101\dots$  ( $4,33333\dots$ )
    - In SSE lab : **DIV\_FIXED64\_signed** (32 predecimal, and decimal, limited accuracy!)

- Problems with Fixed-Point representation:
  - Limited value range
  - Fixed-Point: Compromise between value range and accuracy
- Number representation in the form:  $X = S \cdot M \cdot 2^E$ 
  - Basis: 2
  - **S**: sign → 1-Bit
  - **M**: mantissa → unsigned fixed-point
  - **E**: Exponent (variable) → signed integer
- Very high precision with small numbers
- Very large value range for large numbers (with lower precision)
- Floating point representations are approximations!

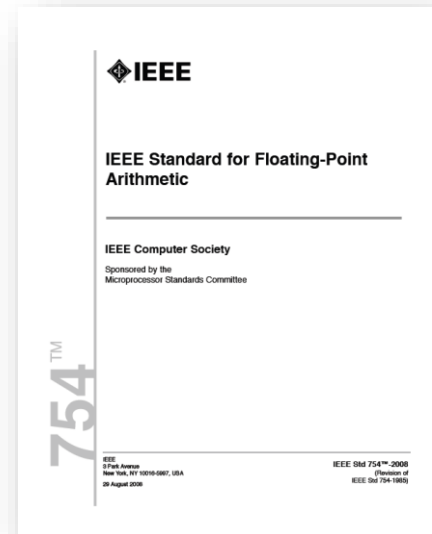- Example: Number 5 in floating point form
  - $5 = +1 \cdot 1.25 \cdot 2^2$
  - $S = 0$
  - $M = 0b1,01\_0000\_0000\_0000\_0000\_0000$
  - $E = 0b00000010$
- But also:  $5 = +1 \cdot 0.625 \cdot 2^3$ ,  $5 = +1 \cdot 0.3125 \cdot 2^4$ ,  $5 = +1 \cdot 0.15625 \cdot 2^5$ , ...
- The floating-point representations are not uniquely determined
- → Normalization of the value range of **Mantissa**
- e.g.  $1 \leq M < 2$


- The exponent of a floating point number is signed
- Hardware required for signed operations
- Storing the exponent as  $E' = E + B$  as an unsigned number
  - B: Bias
  - Example: 8-bit Exponent:  $B=127$
- Enables use of unsigned arithmetic components for floating point units


- Defines floating point number formats and their representation in bits.



	Bits	Mantissa (Bit)	Exponent (Bit)	Bias	Value range	Accuracy (Decimal)
Single (float)	32	23	8	127	$10^{-38}$ bis $10^{38}$	$\approx 7$
Double	64	52	11	1023	$10^{-308}$ bis $10^{308}$	$\approx 16$




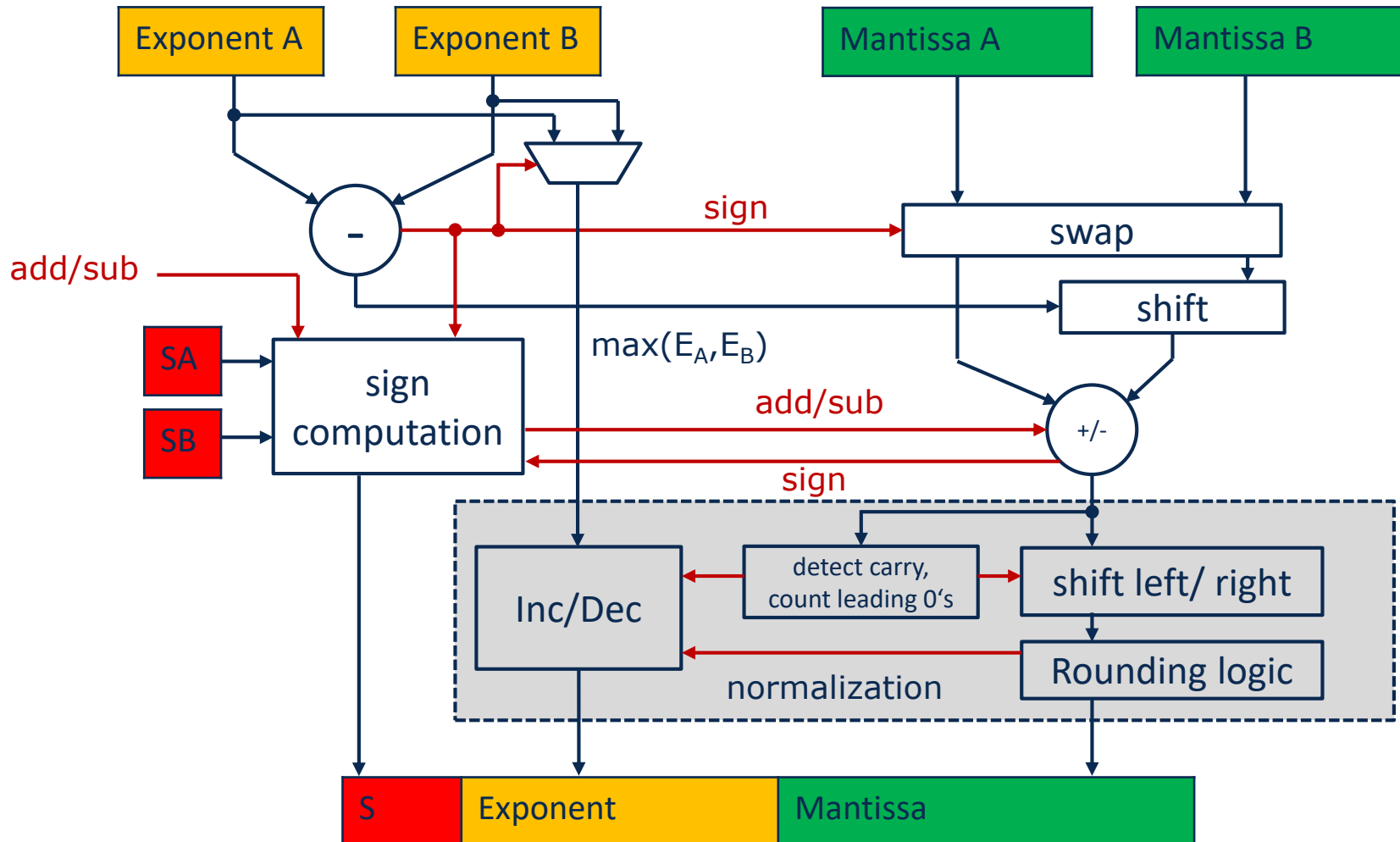


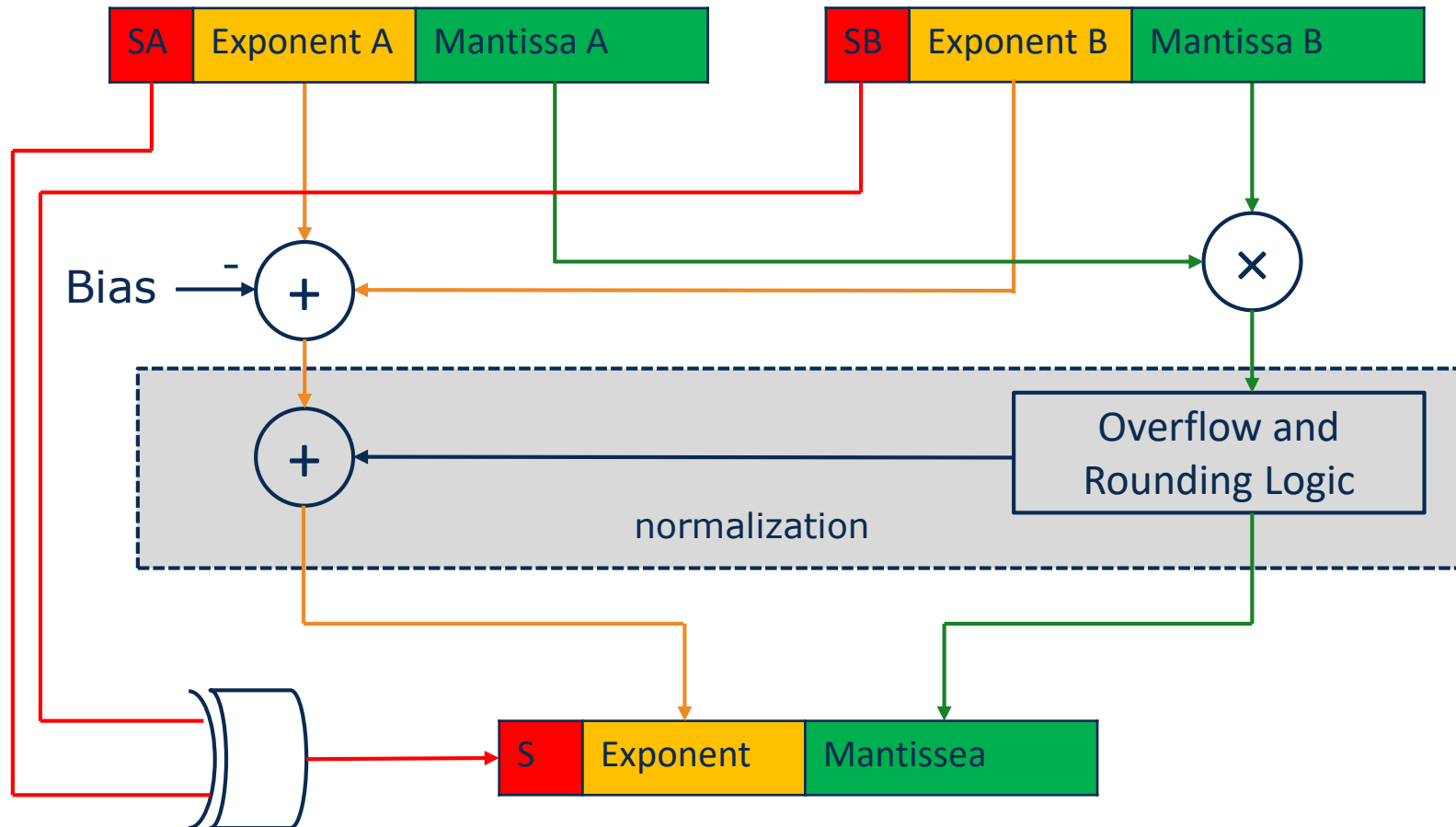

- Number formats fixed-point (signed, unsigned) and floating point
- Higher accuracy requires more effort regarding:
  - Higher storage requirements
  - Larger chip area for arithmetic
  - Longer logic runtimes → Frequently implementing complex arithmetic blocks in several clock cycles (pipelining)
  - Higher energy expenditure of the calculation
- Choice of number format is critical to the efficiency of hardware implementation
  
# Arithmetic - Circuits

- Addition of 2-bit
  - Inputs A, B
  - Output S (Sum), CO (Carry)




A	B	S	CO
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \oplus B$$

$$CO = A \cdot B$$

 - Addition of 2 bit and Carry
  - Inputs A, B, CI (Carry In)
  - Outputs S (Sum), CO (Carry)




A	B	CI	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A \oplus B \oplus CI$$

$$CO = A \cdot B + CI \cdot (A \oplus B)$$


$$S = A \oplus B \oplus CI$$
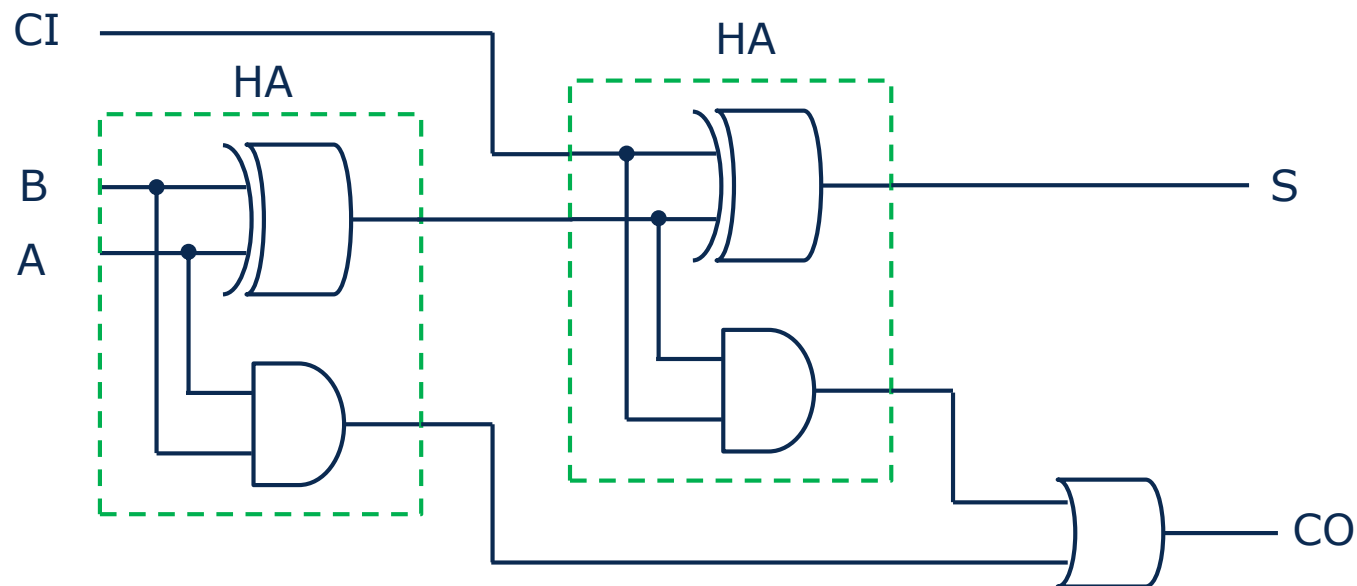
$$CO = A \cdot B + CI \cdot (A \oplus B)$$



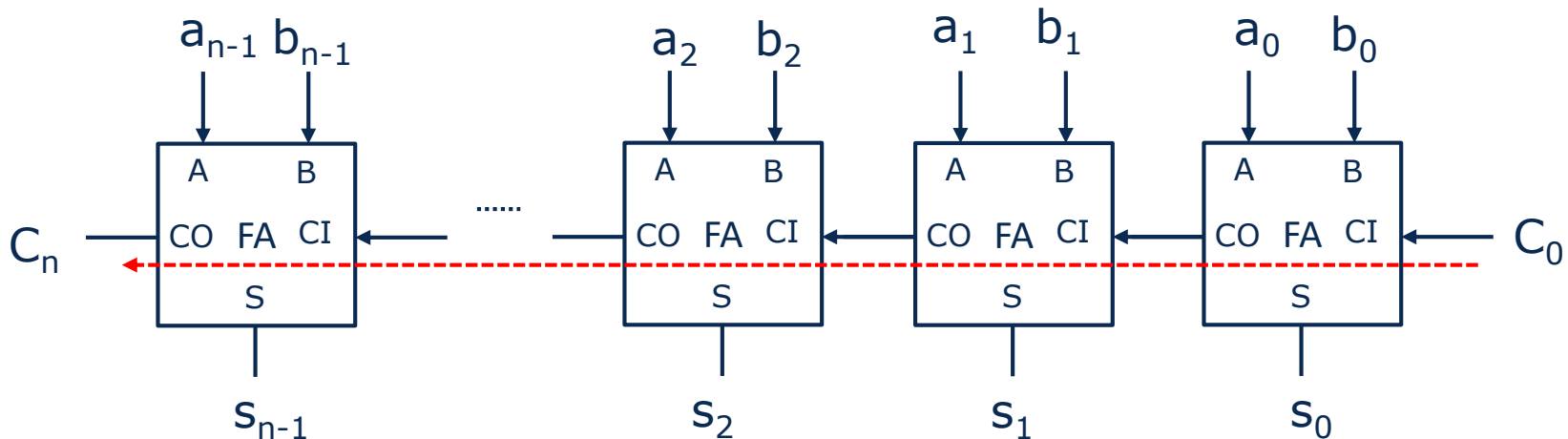**Carry path CI → CO: 2 gate stages**

- Concatenation of full adders to add n-bit numbers
- If no CI is needed, first stage can be replaced with HA



**Critical path: CI → CO: 2\*n gate stages**

- Example:
  - 32-Bit Adder → 64 gate delays
  - 28nm:  $t_{\text{gate}} \approx 50\text{ps} \rightarrow T = 3,2\text{ns} \rightarrow f_{\text{max}} \approx 310\text{MHz}$
- State of the art: 32-bit processors at > 2GHz → **How does it work?**



- Carry paths are time critical!
- → Reduction of the logic levels in the carry path
- Introduce new values:
  - P: Propagate: Passing on the carry
  - G: Generate: Generating the carry

A	B	CI	S	CO	P	G
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	1	0	1	0
0	1	1	0	1	1	0
1	0	0	1	0	1	0
1	0	1	0	1	1	0
1	1	0	0	1	0	1
1	1	1	1	1	0	1

$$S = A \oplus B \oplus CI$$

$$CO = A \cdot B + CI \cdot (A \oplus B)$$

$$P = A \oplus B$$


$$G = A \cdot B$$

$$S = P \oplus CI$$


$$CO = G + CI \cdot P$$

- Prediction of carry bits → Carry Look Ahead
- Example  $n=4$ :
  - $C_1 = G_0 + C_0 P_0$
  - $C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$
  - $C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$
  - $C_4 = G_3 + C_3 P_3 = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$


**Requires only 5 logic stages!**

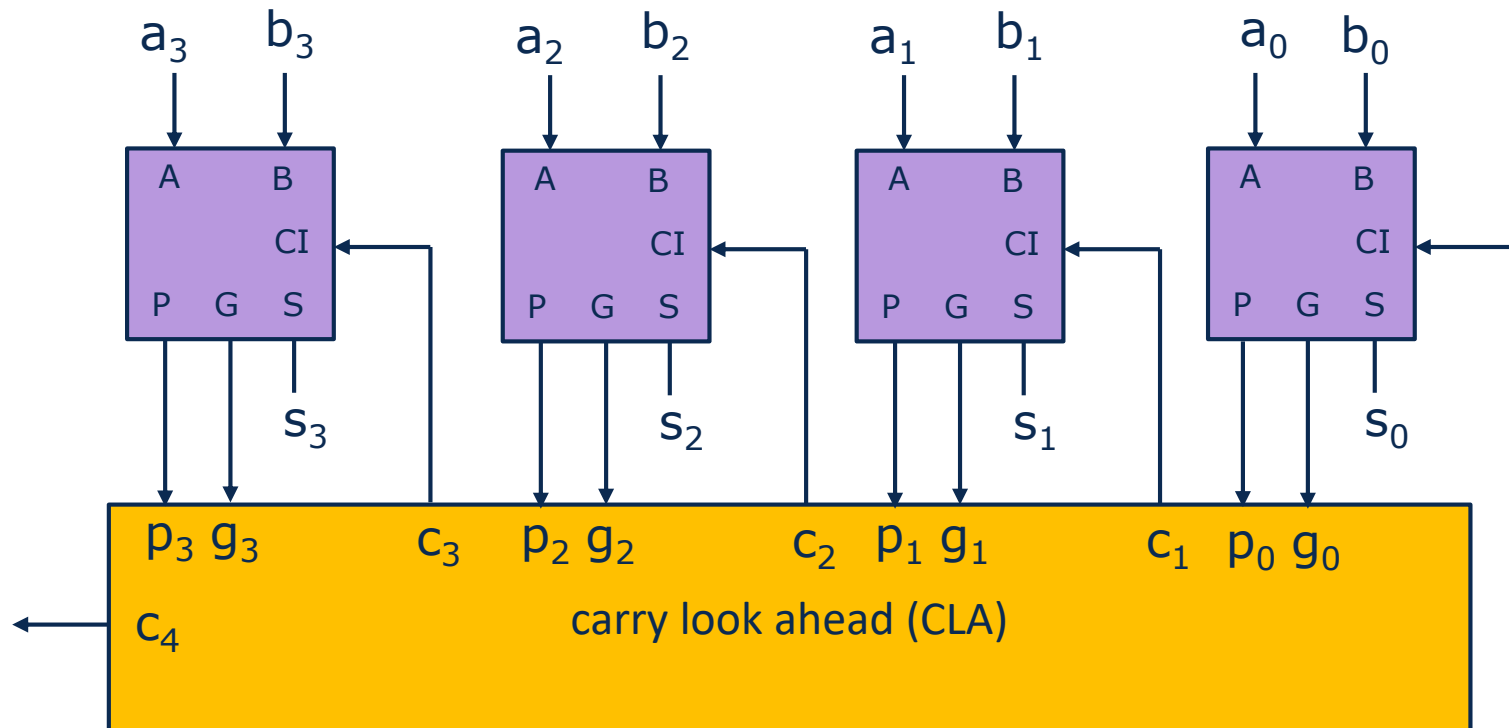
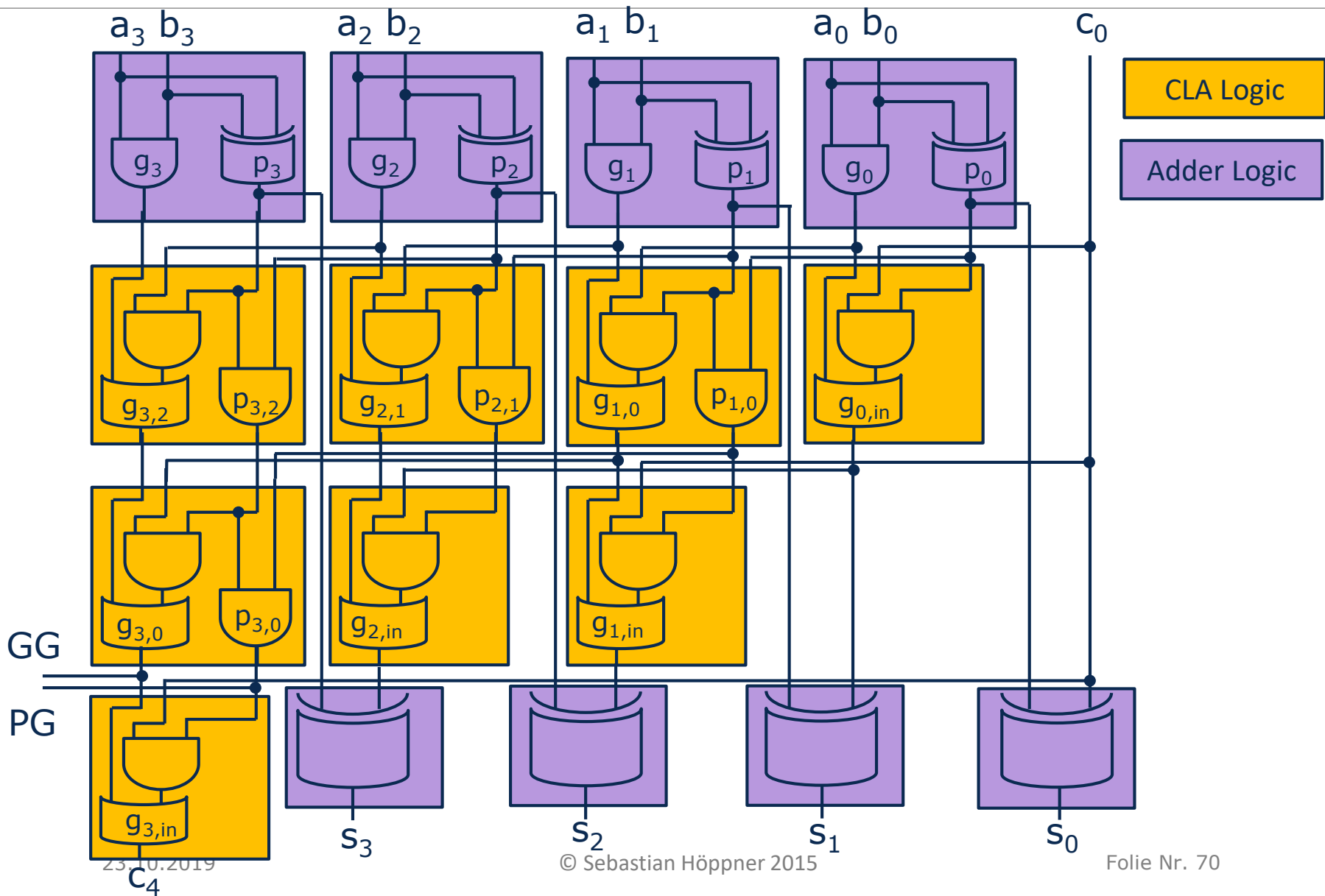
# Carry Look Ahead Logic: „Kogge Stone Adder“





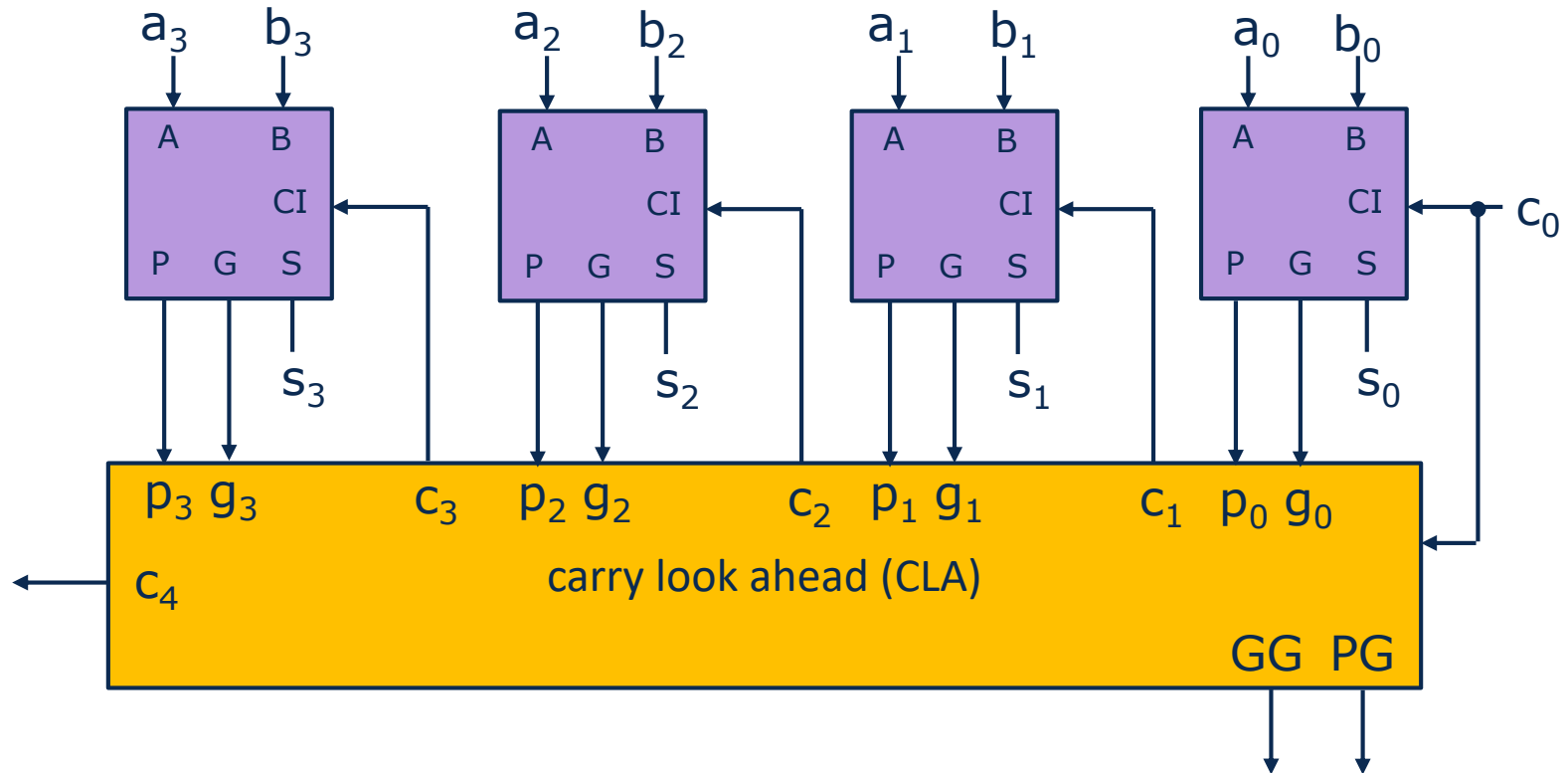- Pre-calculation of Generate and Propagate for an n-bit group




- Group Propagate:  $PG = P_3 P_2 P_1 P_0$  → 2+1 gate stages
- Group Generate:  $GG = G_3 + G_2 P_3 + G_1 P_3 P_2 + G_0 P_3 P_2 P_1$  → 4+1 gate stages


## 4-Bit CLA Adder

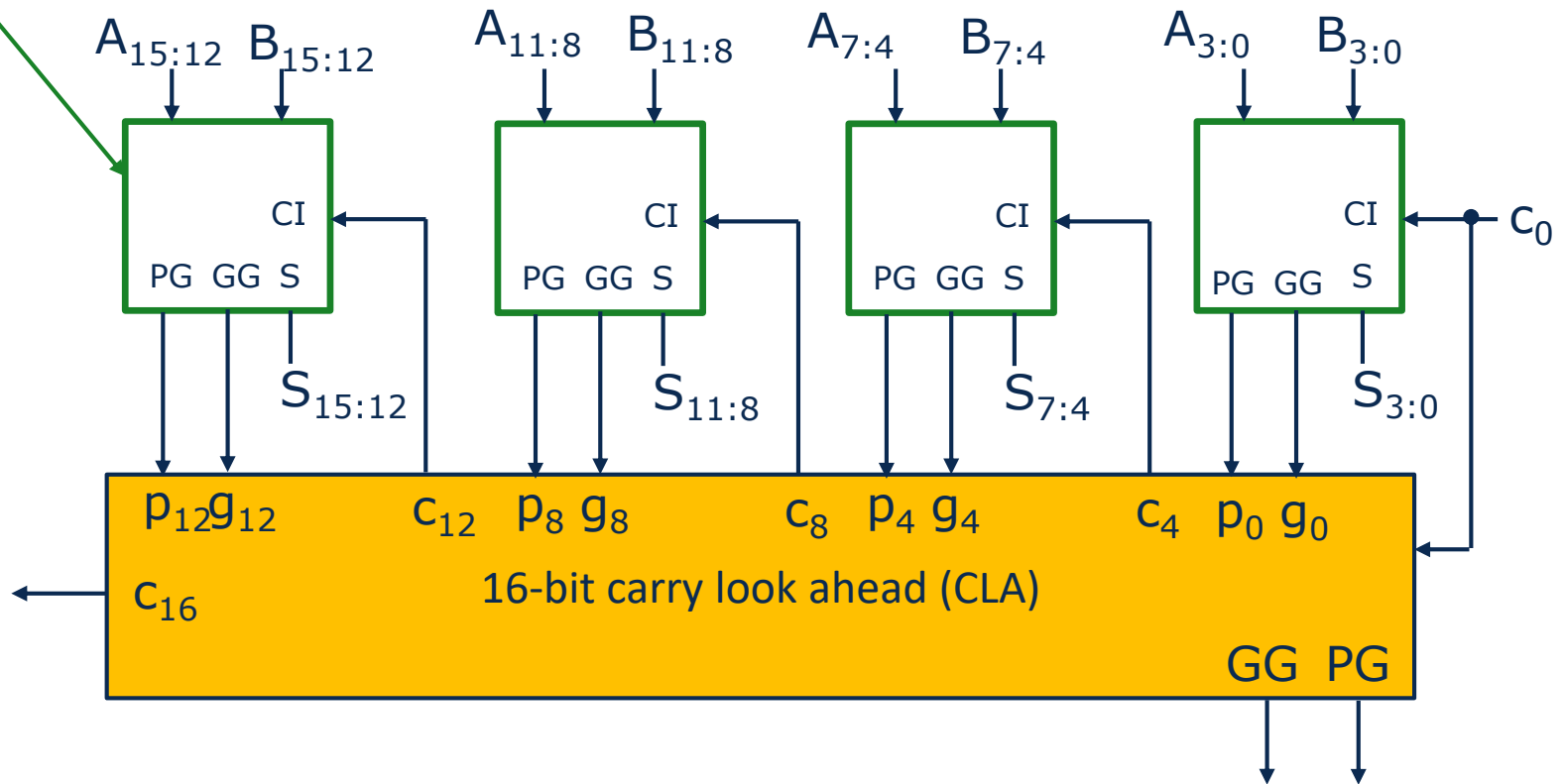 


## 4-Bit CLA Adder

 


## 16-Bit CLA Adder

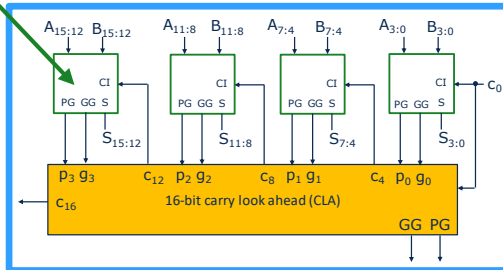


## 64-Bit CLA Adder

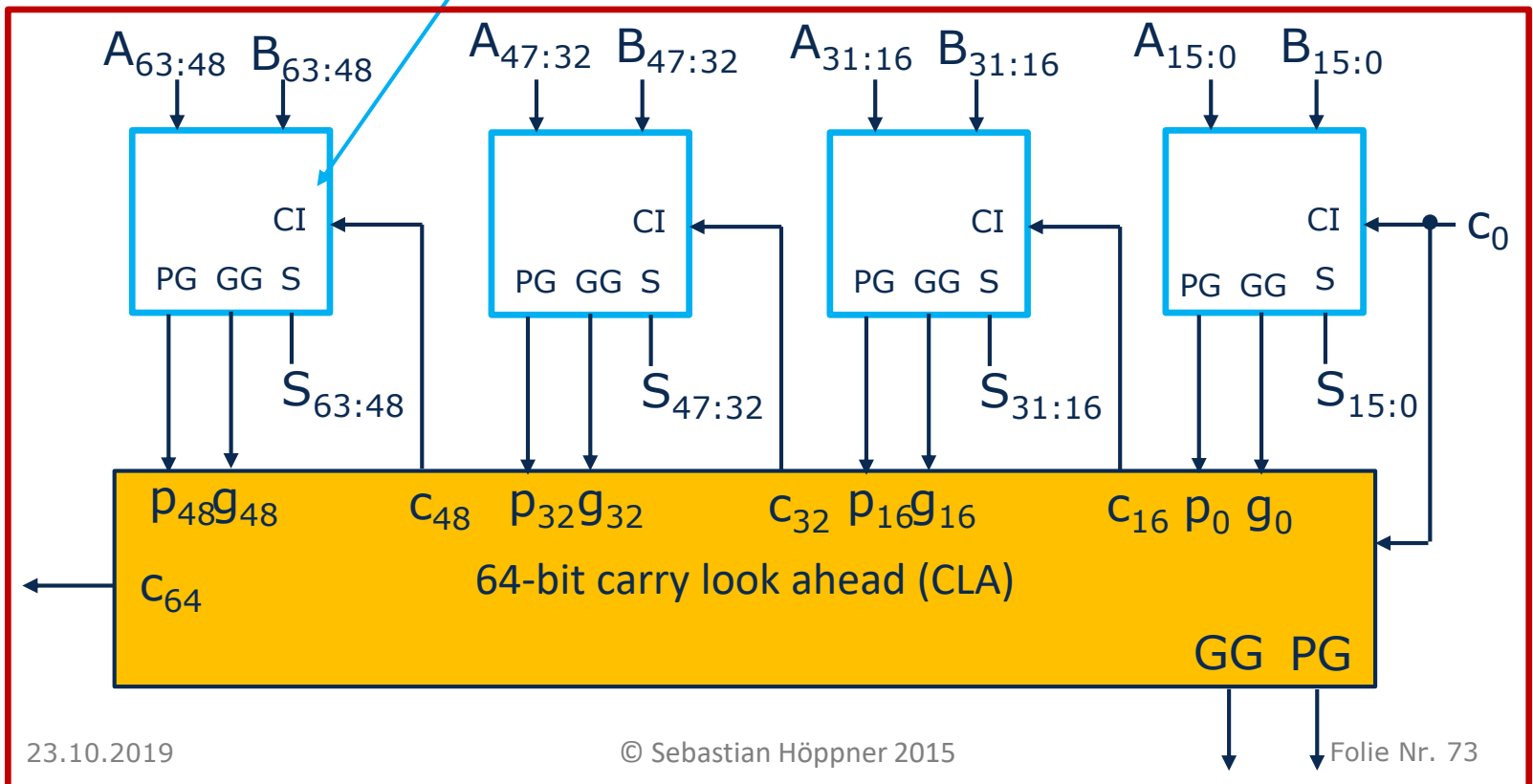

 


4-Bit CLA Adder

Carry Path (G)  
4 gate stages

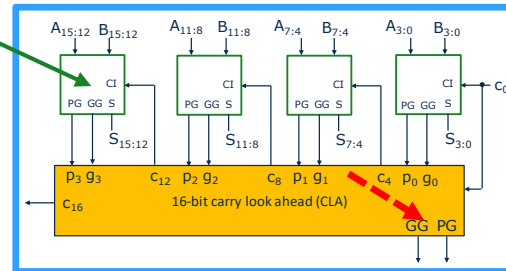

16-Bit CLA Adder

Carry Path (G) 4 gate stages

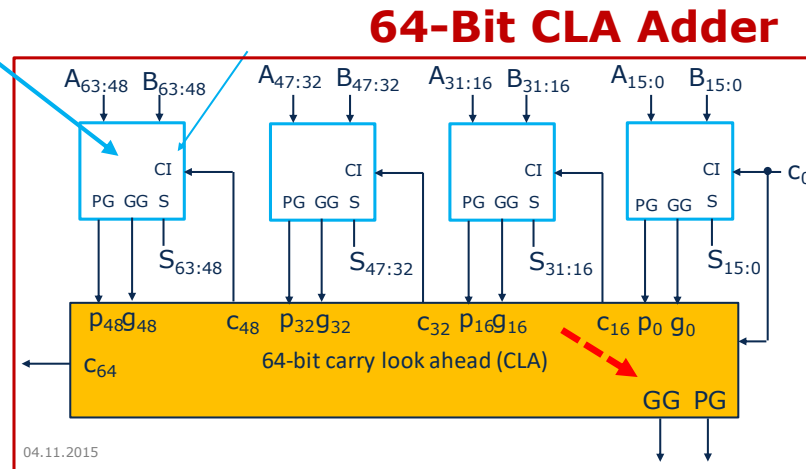

64-Bit CLA Adder

Carry Path (G) 4 gate stages


- $\rightarrow 1 + 3 \cdot 4 + 2 = 15$  gate stages for C64
- 64-Bit Ripple Carry Adder would have  $\approx 128$  gate stages



- Fast carry forwarding through multiplexer
- Homogeneous hardware implementation of adder chains

$$S = P \oplus CI$$

$$CO = G + CI \cdot P$$

 

**Carry Path CI → CO: 1 Multiplexer**

- Fast carry paths in Field-Programmable Gate Arrays (FPGAs)
- Implementing fast adders and subtractors with configurable word length

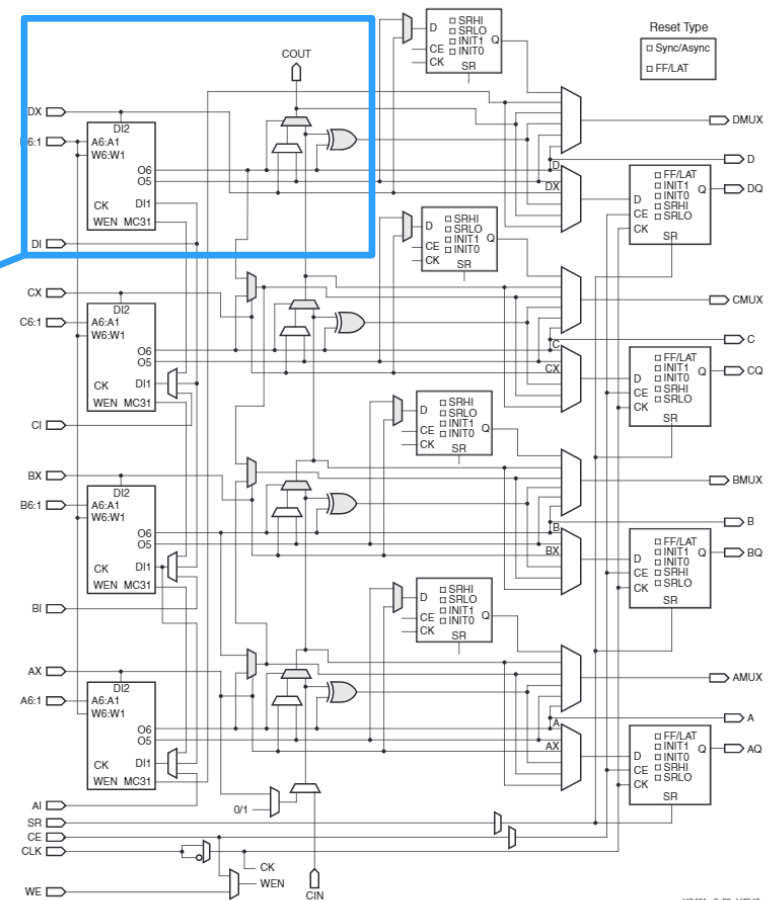
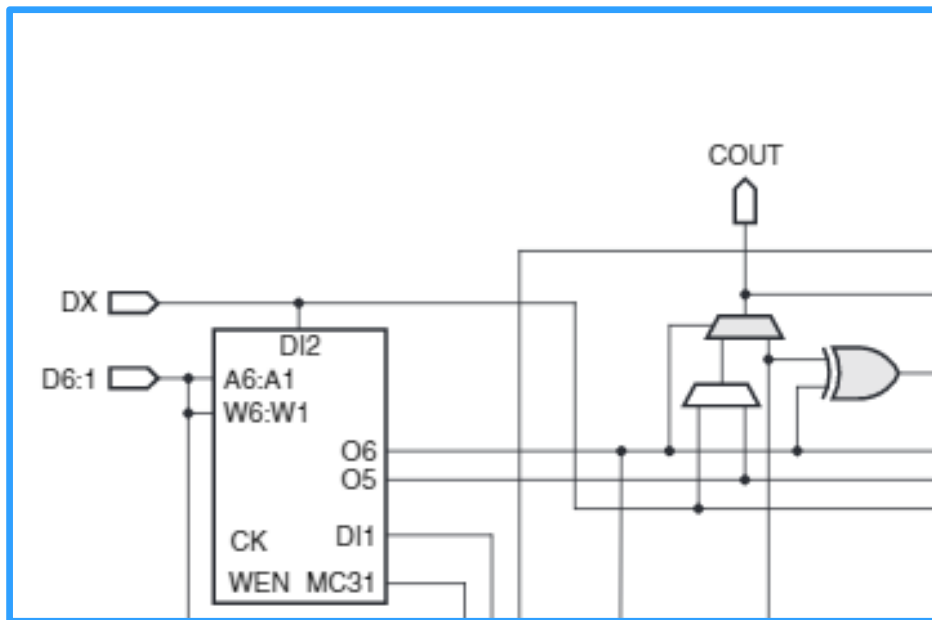



Figure 2-3: Diagram of SLICEM

- Source: Xilinx 7 Series FPGAs Configurable Logic Block, User GuideUG474 (v1.7) November 17, 2014

- Weighted addition of partial products  $a_i \cdot b_j$


					<b>A3</b>	<b>A2</b>	<b>A1</b>	<b>A0</b>	
					A3B0	A2B0	A1B0	A0B0	<b>B0</b>
+				A3B1	A2B1	A1B1	A0B1		<b>B1</b>
+			A3B2	A2B2	A1B2	A0B2			<b>B2</b>
+		A3B3	A2B3	A1B3	A0B3				<b>B3</b>
	<b>P7</b>	<b>P6</b>	<b>P5</b>	<b>P4</b>	<b>P3</b>	<b>P2</b>	<b>P1</b>	<b>P0</b>	

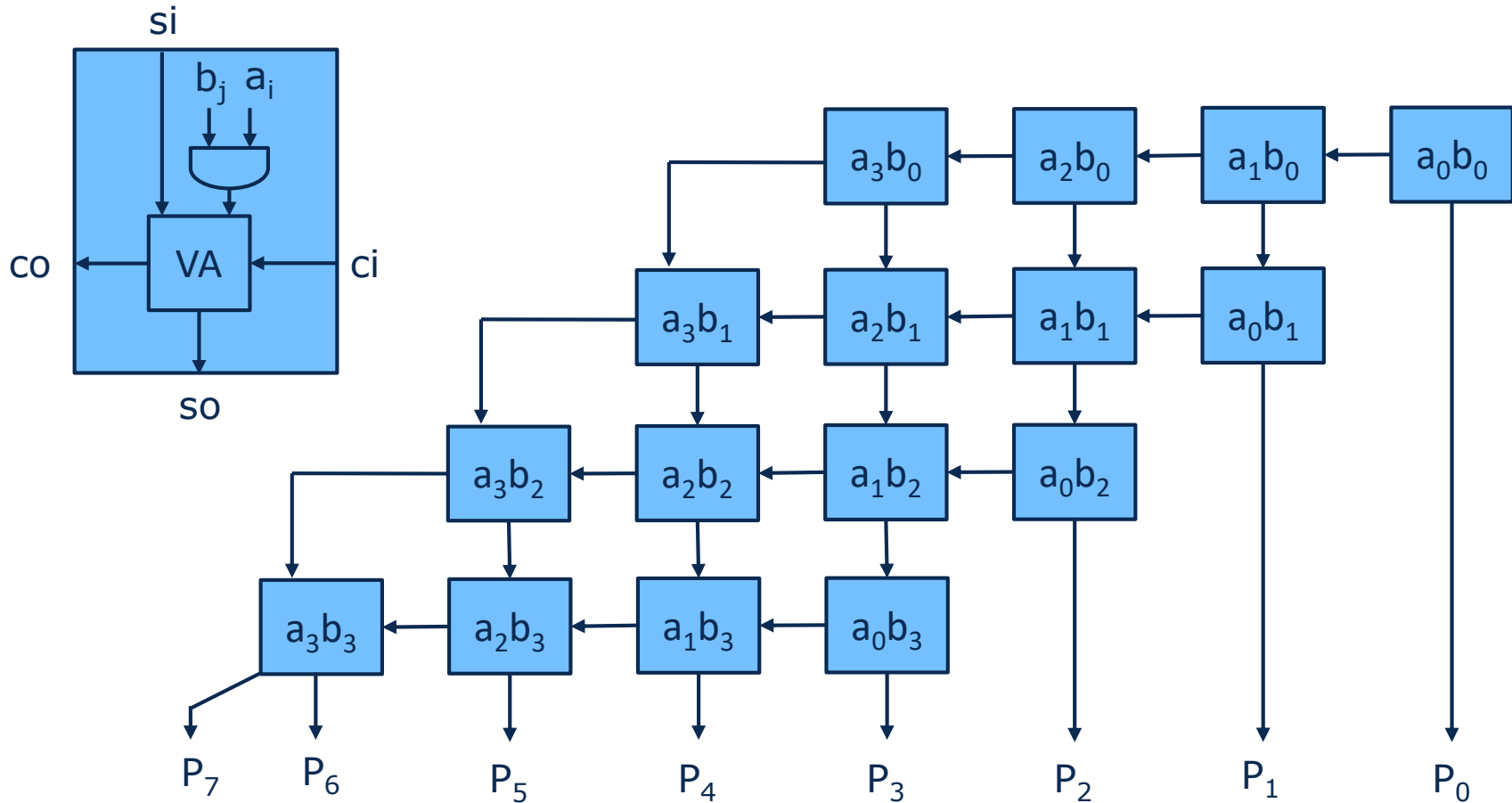- Addition of partial products  $a_i \cdot b_j$  by ripple carry chains




- Addition of the **weighted** partial products in a tree structure Reduction of the logic levels especially for large adders (complexity  $O(\log n)$ )

					A3	A2	A1	A0	
					A3B0	A2B0	A1B0	A0B0	B0
+				A3B1	A2B1	A1B1	A0B1		B1
+			A3B2	A2B2	A1B2	A0B2			B2
+	A3B3	A2B3	A1B3	A0B3					B3
	P7	P6	P5	P4	P3	P2	P1	P0	

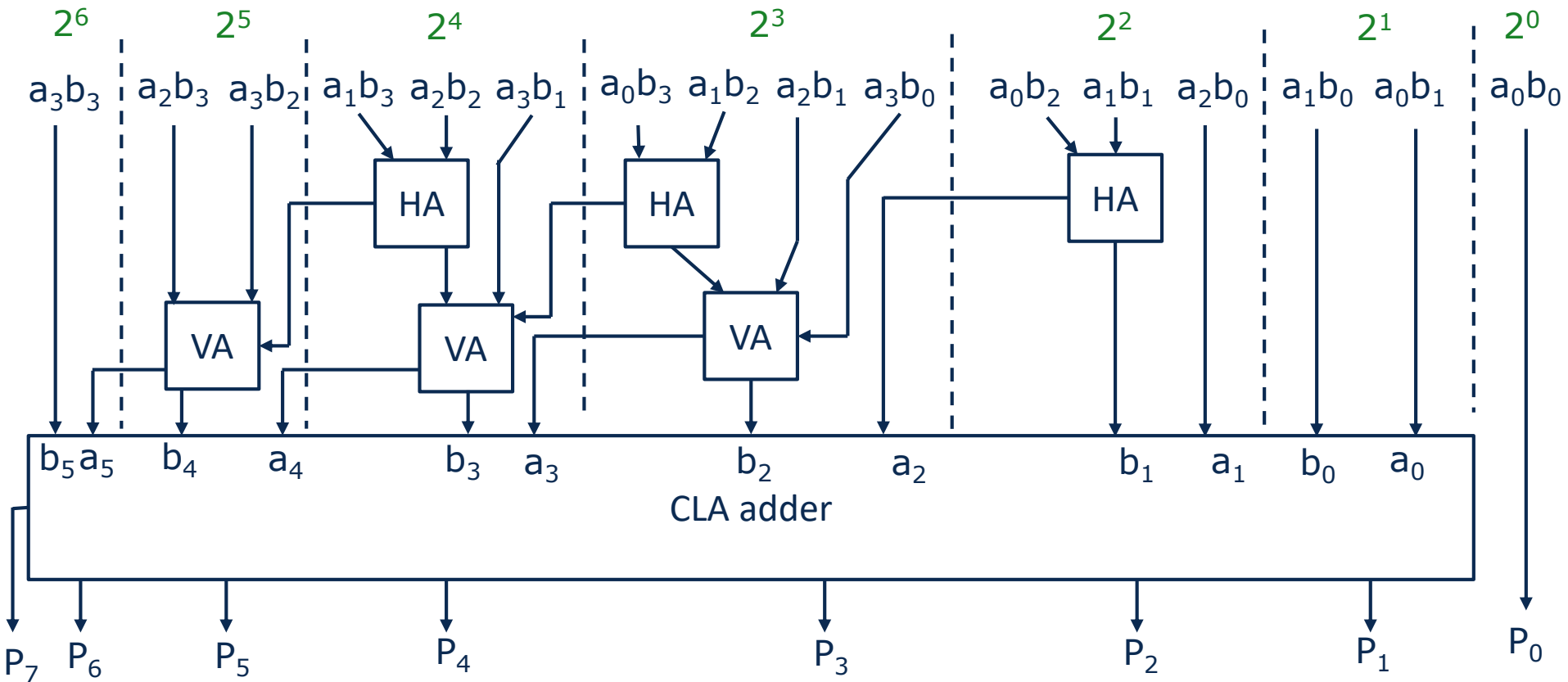


- Presentation of circuits for binary addition and multiplication
- Strategies for optimizing hardware implementation regarding gate delays
- In the practical implementation further boundary conditions are to be considered, such as e.g. chip area, power consumption

# Data Paths



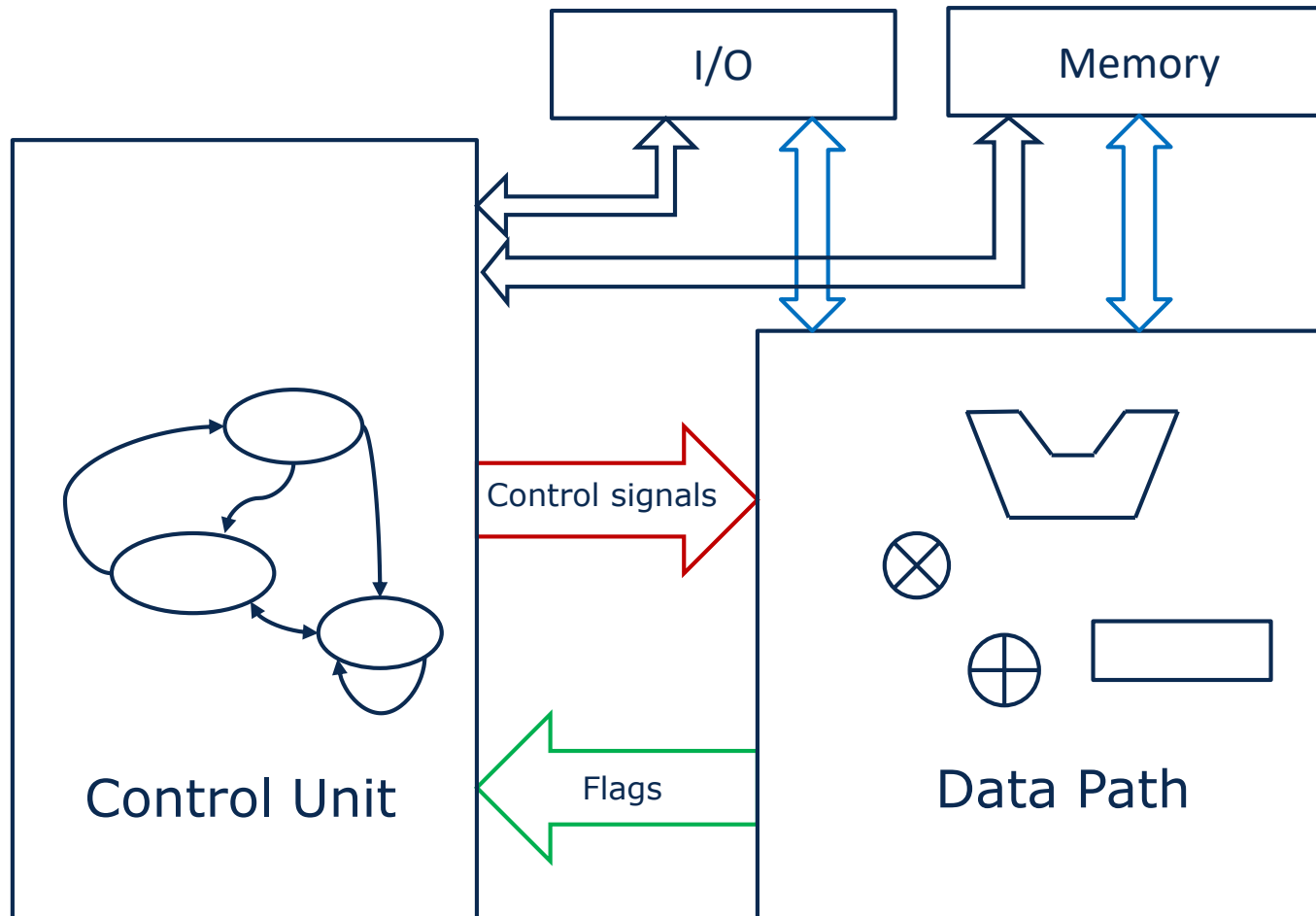




- Arithmetic Logic Unit (ALU) process numerical and logic data
  - Operands (OPA, OPB, ...)
  - Mode (M): Choice of operation, e.g.
    - ADD, SUB, MUL, DIV, SHIFT, AND, OR, ...)
  - Result (RES)
  - Status Flags (F): Additional information about the operation, e.g.
    - CARRY, OVERFLOW, SIGN, ZERO
- ALU data path building blocks can be combinational or sequential
- In SSE Lab, dedicated building blocks are available for the arithmetic operations


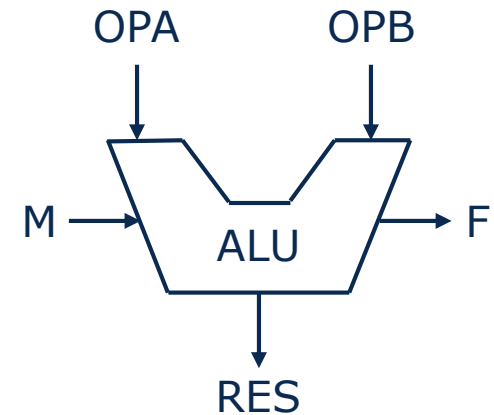


 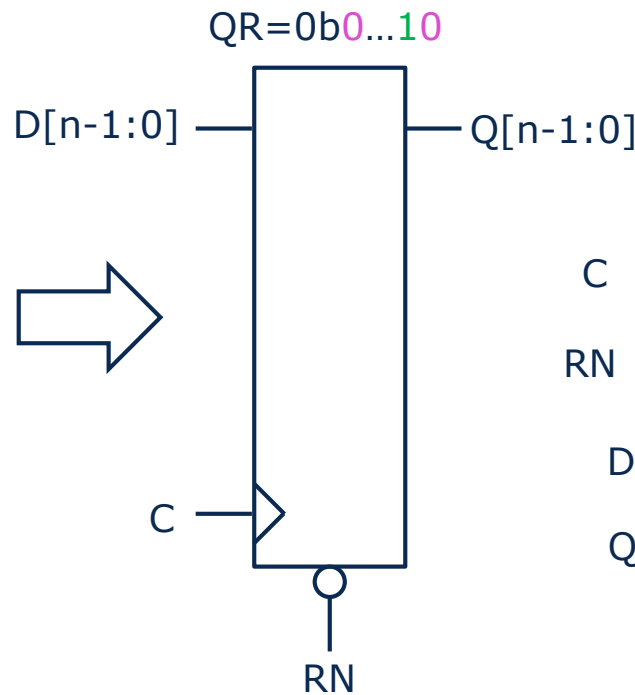 - Ordering n-bit flip-flops for data storage
- **Reset-value** of register, set at implementation time by selecting the flip-flop type (**Set, Reset**)





Very fast access (1 clock), very short delay CLK  $\uparrow$   $\rightarrow$  Q

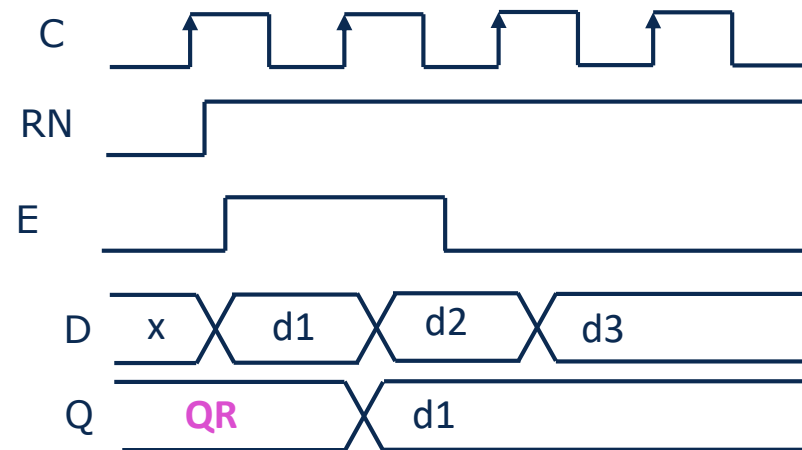 - Conditional writing to flip-flop when  $E = 1$
- $Q_{i+1} = D_i$ , when  $E = 1$ 
  - $Q_{i+1} = Q_i$ , otherwise
- Implementation using **Multiplexer**
  - Permanent data writing
  - Selection of data




- Low circuit complexity
- Hardly any increase in power consumption with high write activity

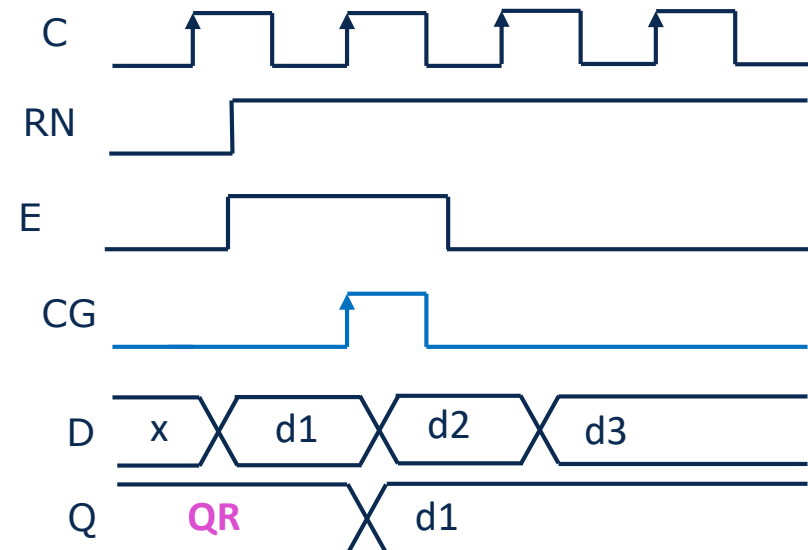 - Implementation using **Clock Gate**
  - Selective clocking for the register




 - Higher circuit complexity (area)
- Higher power consumption with high write activity
- Lower power consumption with low write activity



- → Clock Gating application depends on the operation scenario



- Addressable memory
- Memory Array
  - Data word length:  $n_D$
  - Addresses:  $n_A$
  - Capacity  $n_A \cdot n_D$
- Access via ports
  - Write:  $\text{MEM}(\text{addr}) = D_{\text{IN}}$
  - Read:  $Q = \text{MEM}(\text{addr})$
- Criteria:
  - Storage density [ $\text{Bit}/\mu\text{m}^2$ ]
  - Access time (number of clock cycles, delay  $\text{CLK} \rightarrow Q$ )
  - Power consumption
  - Non-volatile memory (yes/no)

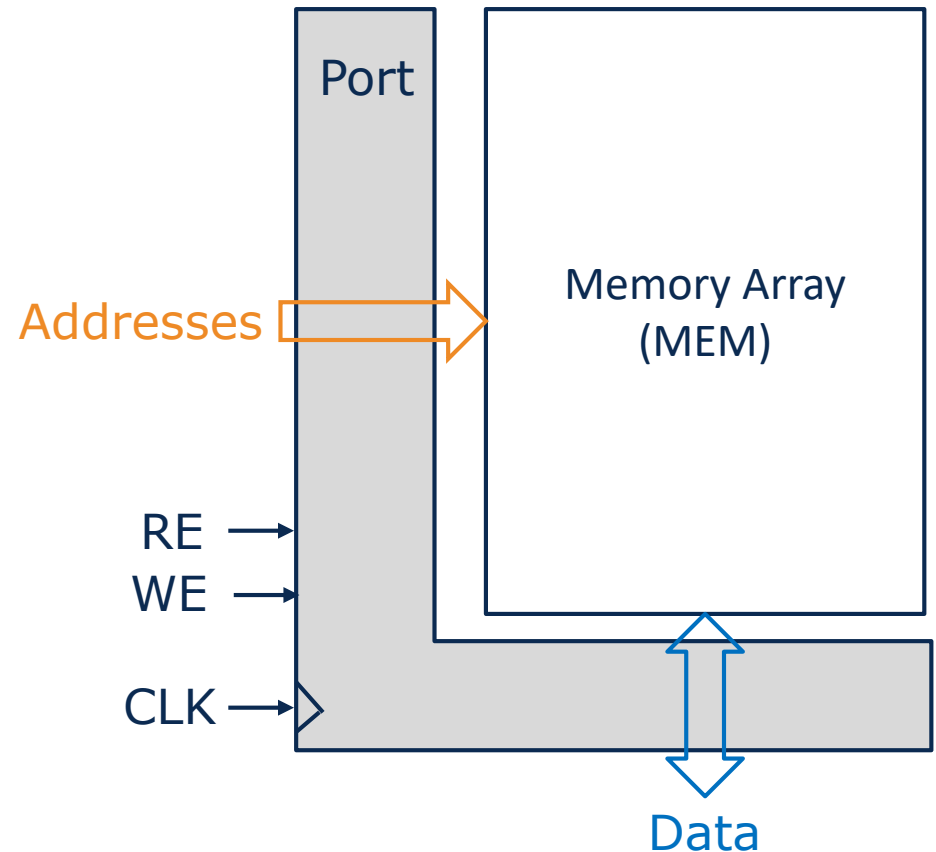

Type	NVM	Bits/ $\mu\text{m}^2$	Access time	Typical memory sizes	Comments
Latch	No	<1	some 10ps	some Bits	Control circuit needed bec. level sensitive!
FlipFlop	No	<0.4	some 10ps	some Bits	
SRAM	No	<7 (Cell) <5 (Macro)	some 100ps	some kBit to MBit	Complex control circuit (SRAM Macro)
(embedded) DRAM	No	<30	some 100ps	some kByte to Mbyte	Dynamic memory, refresh needed. Possibly extra process options (costs!)
(embedded) Flash	Yes	<30	some ns	some kByte to Mbyte	Extra process options (costs!)
ROM	Yes	<15	some 100ps	some kBit to MBit	„Mask programming“ during implementation
OTP	Yes	<10	some 100ps	some kBit to MBit	„one-time programming“ when testing the chip


Values estimated for 28nm technology node

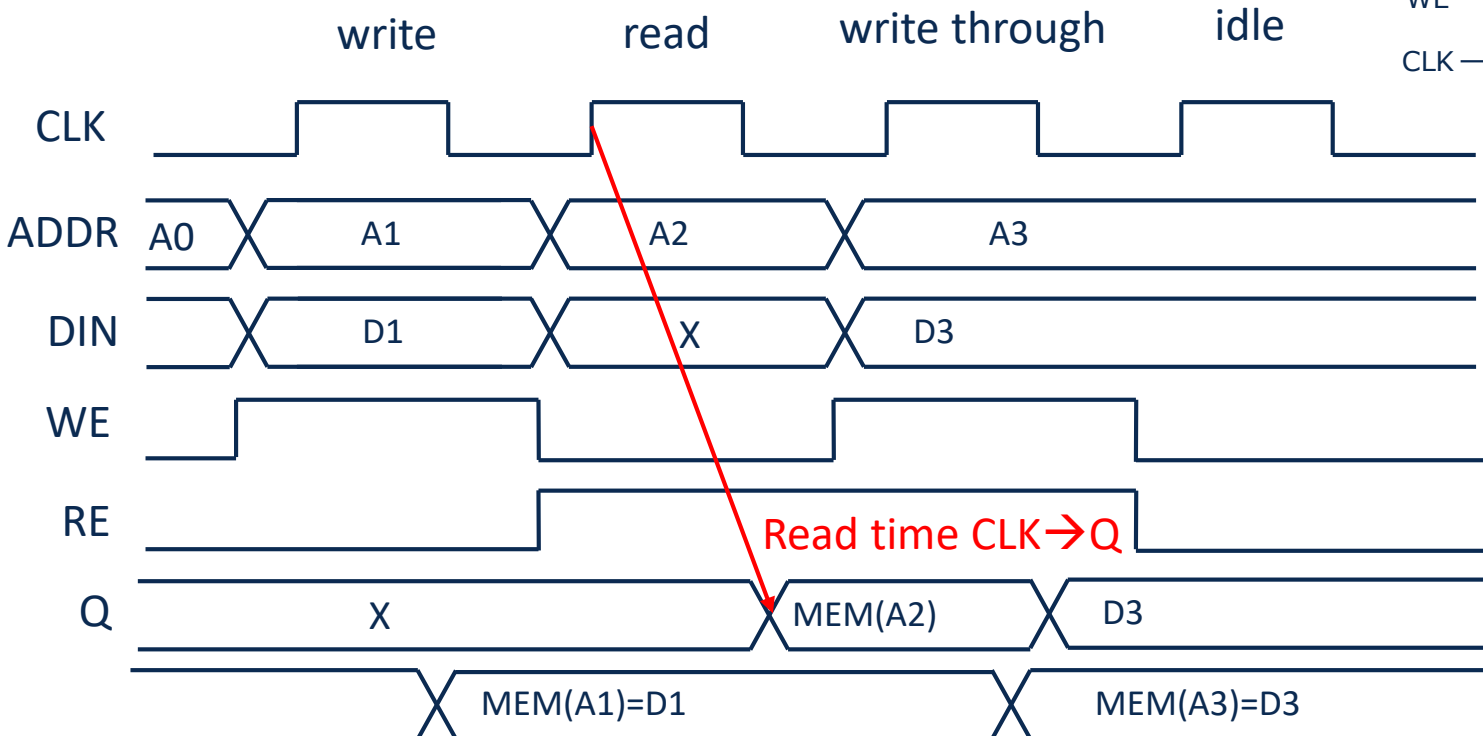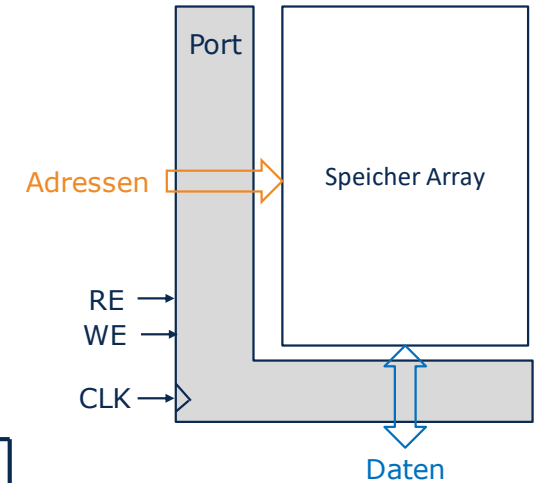- Example:
  - Synchronous SRAM Port
  - 1 clock access time
  - Write-Through Function







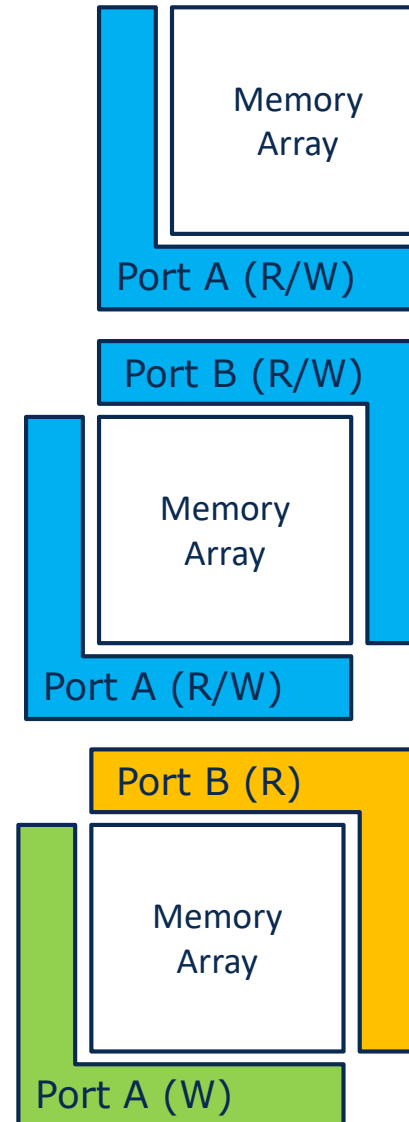- Single Port (SP)
  - Access from **one Write/Read** Port
- Dual Port (DP)
  - Access from **2 independent Write/Read** Ports
  - Synchronous and asynchronous variants possible
  - Arbitration / prioritization of Write accesses to the same addresses necessary
- Two-Port (TP)
  - Access from **one Write Port** and **one seperated Read Port**



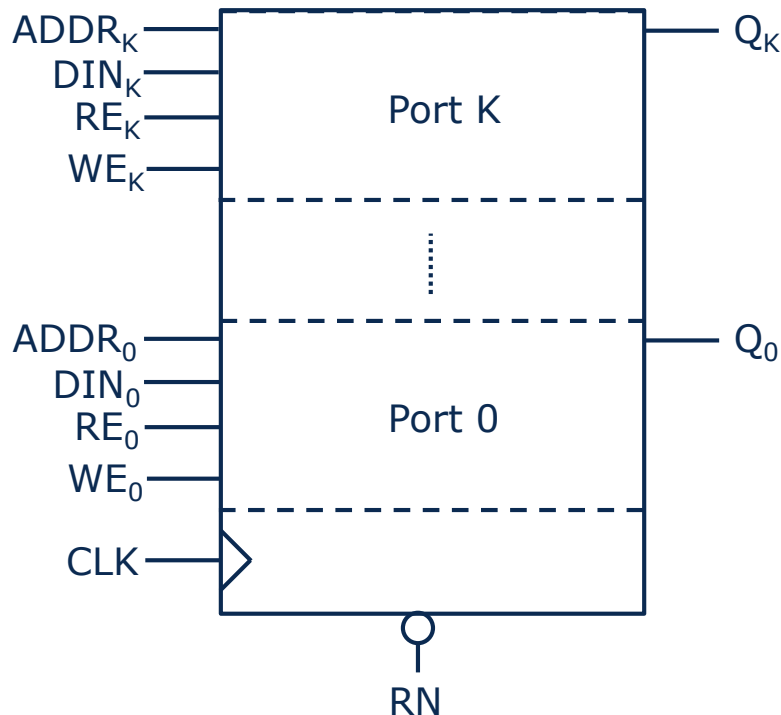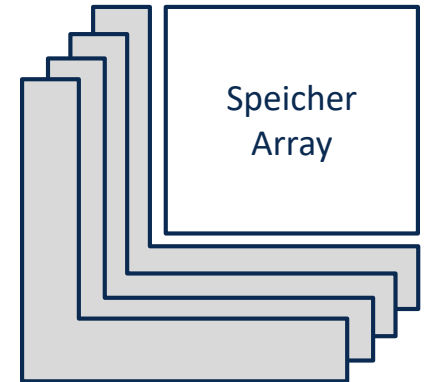- Arrays of registers with multiple write and read ports
- Addressable access
- Typically synchronous (same clock for all ports)
- Faster access (1 Clk), short delay  $CLK \uparrow \rightarrow Q$





- Application in systems with multiple cores



- Register File for Infineon X-GOLD SDR™ 20 Processor
- Developed by the HPSN chair (2008/2009)
- 16-words of 34 bits each, 4-Write Ports, 6 Read Ports
- Cell-Based Design → Optimization at Transistor level



Source: infineon.com

 
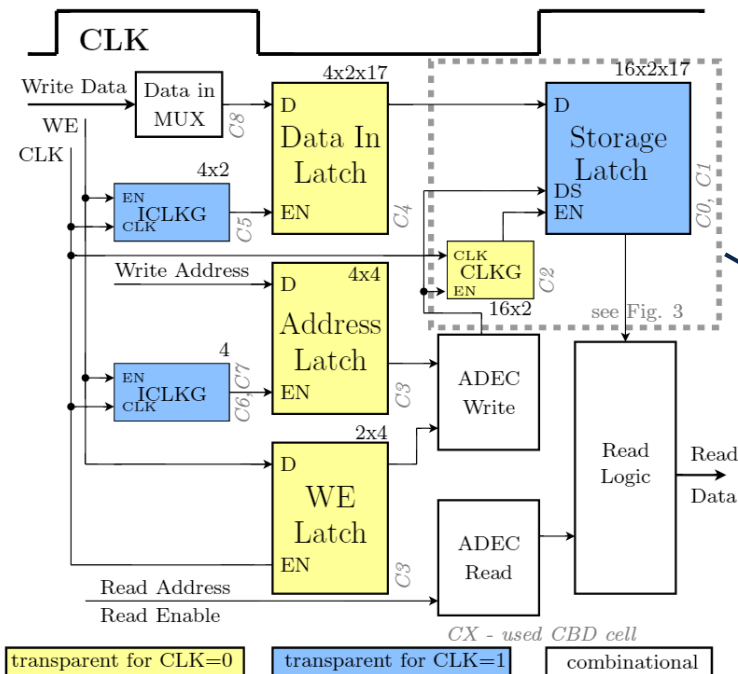


 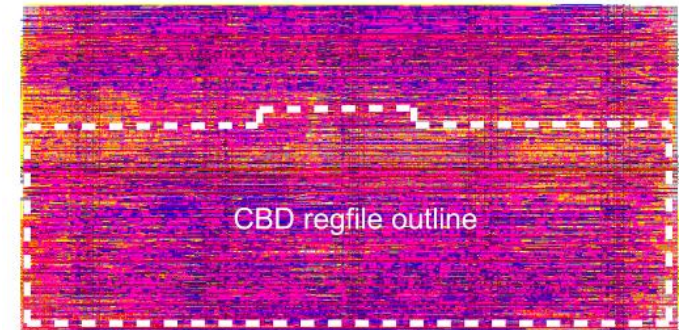- Implementation in 65nm CMOS Technology
- $\approx 0,026\text{mm}^2$  chip area ( $0,02\text{Bit}/\mu\text{m}^2$ )
- 300MHz clock frequency
- Increased efficiency compared to synthesis and place & route implementation:
  - 44% of saved area and
  - 30% of power consumption reduced






- The interconnects of data path blocks should be flexible and reconfigurable
- Bus systems serve the networking (connection) of data path elements
- 3 approaches will be presented:
  - Tri-state Bus
  - Multiplexer Bus
  - Complex bus systems and Network-on-Chip

  
- Gate **outputs** generate 2 logic levels (0,1)



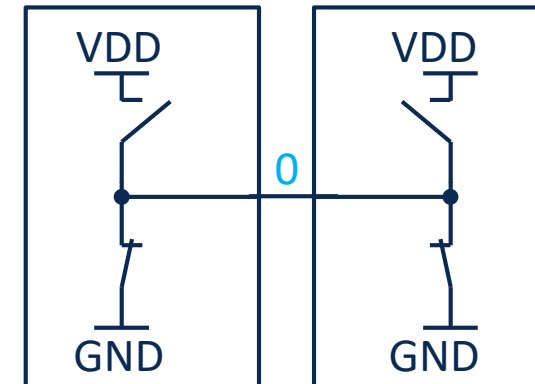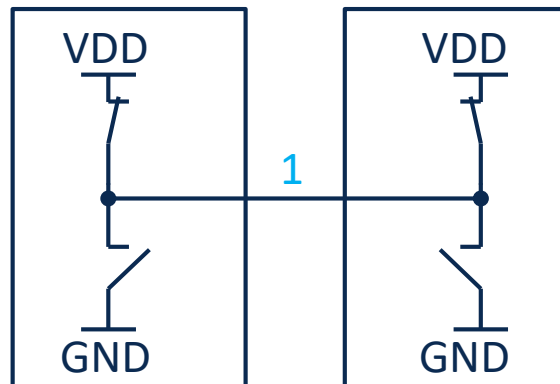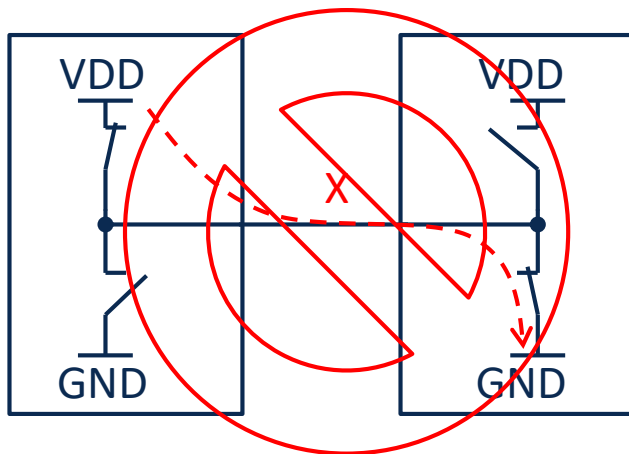
- Connecting several gate **outputs** is only possible if they drive the **same** level



 
- Introducing a **third** initial state (Tri-State) **Z**
- Output driver is switched to high impedance, by separate control signal (OE)



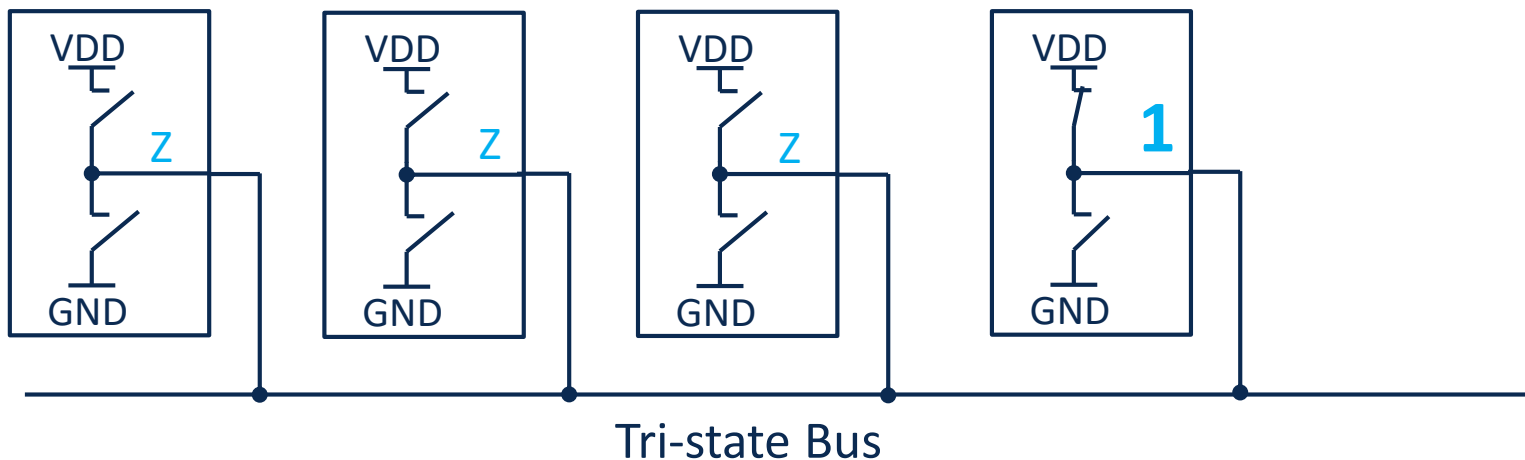- Connecting several gate **outputs** in tri-state is possible.
- Only one driver may be active!



- Buffer with Tri-state output driver

 


OE	A	Z
0	X	Z
1	0	0
1	1	1







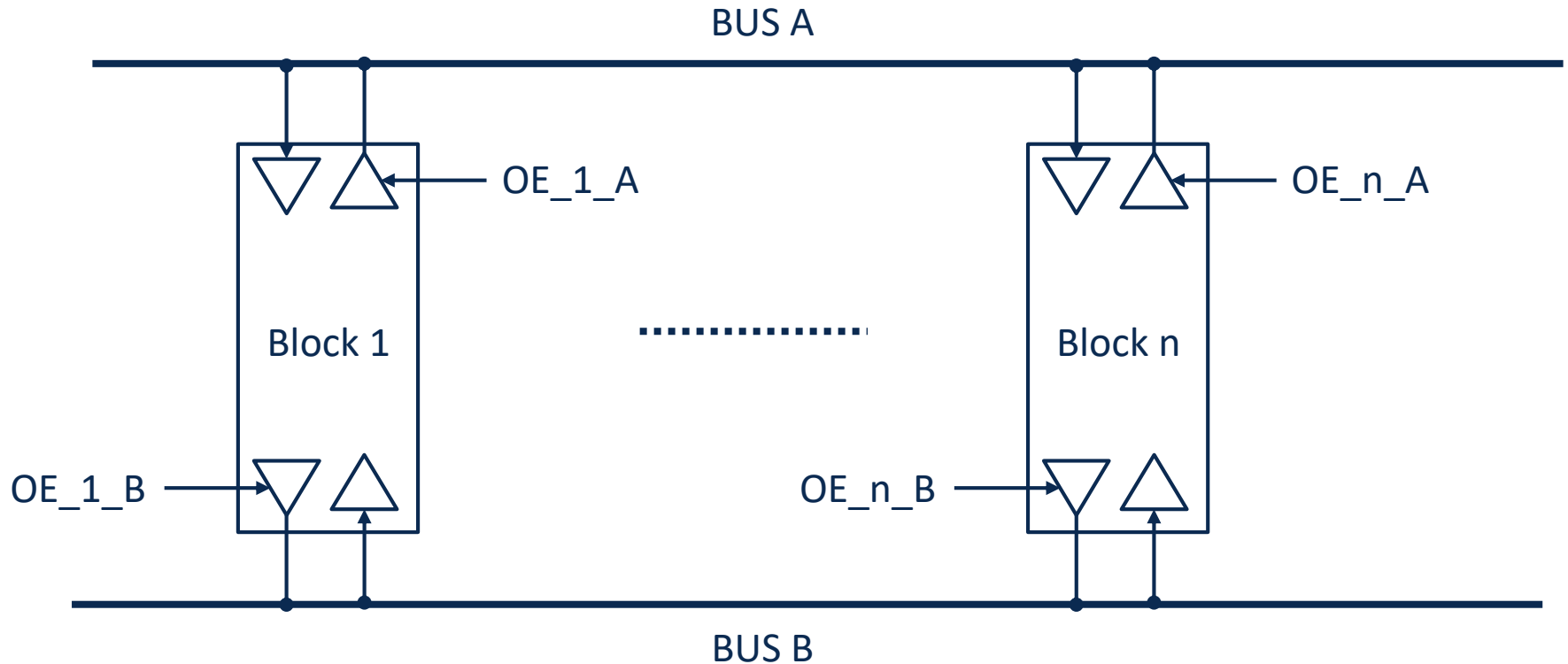- Combinational gates and sequential building blocks (e.g., registers) may be supplied with tri-state outputs.






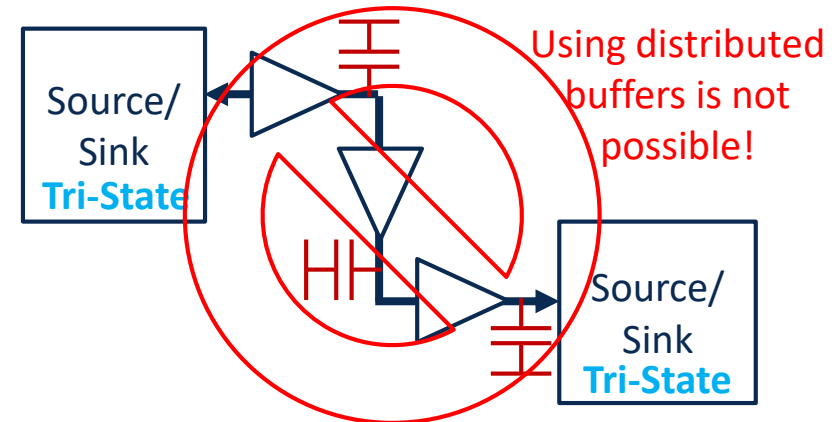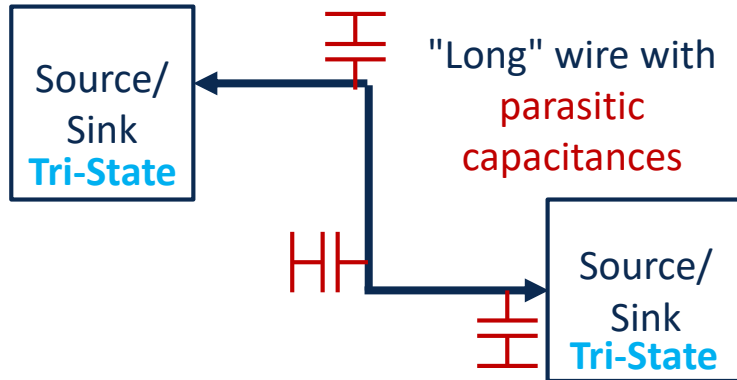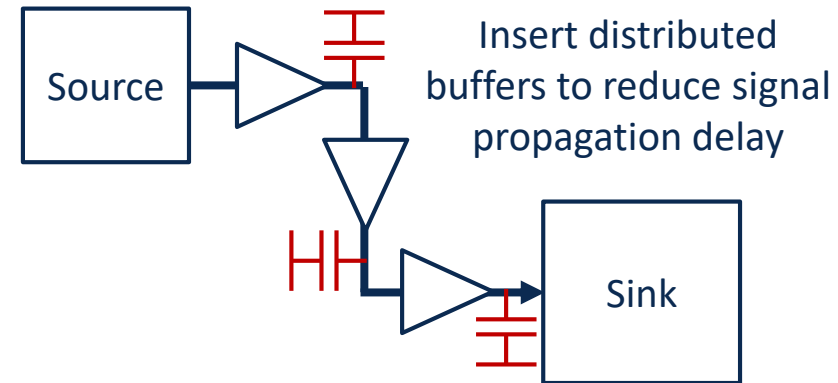 - Several building blocks can be connected to **one** tri-state bus
- Only **one** driver may be active per tri-state bus → Control unit!
- Several buses possible for **parallel** data transfer between building blocks



- In current designs with automated Place & Route (P&R), tri-state signals are avoided!

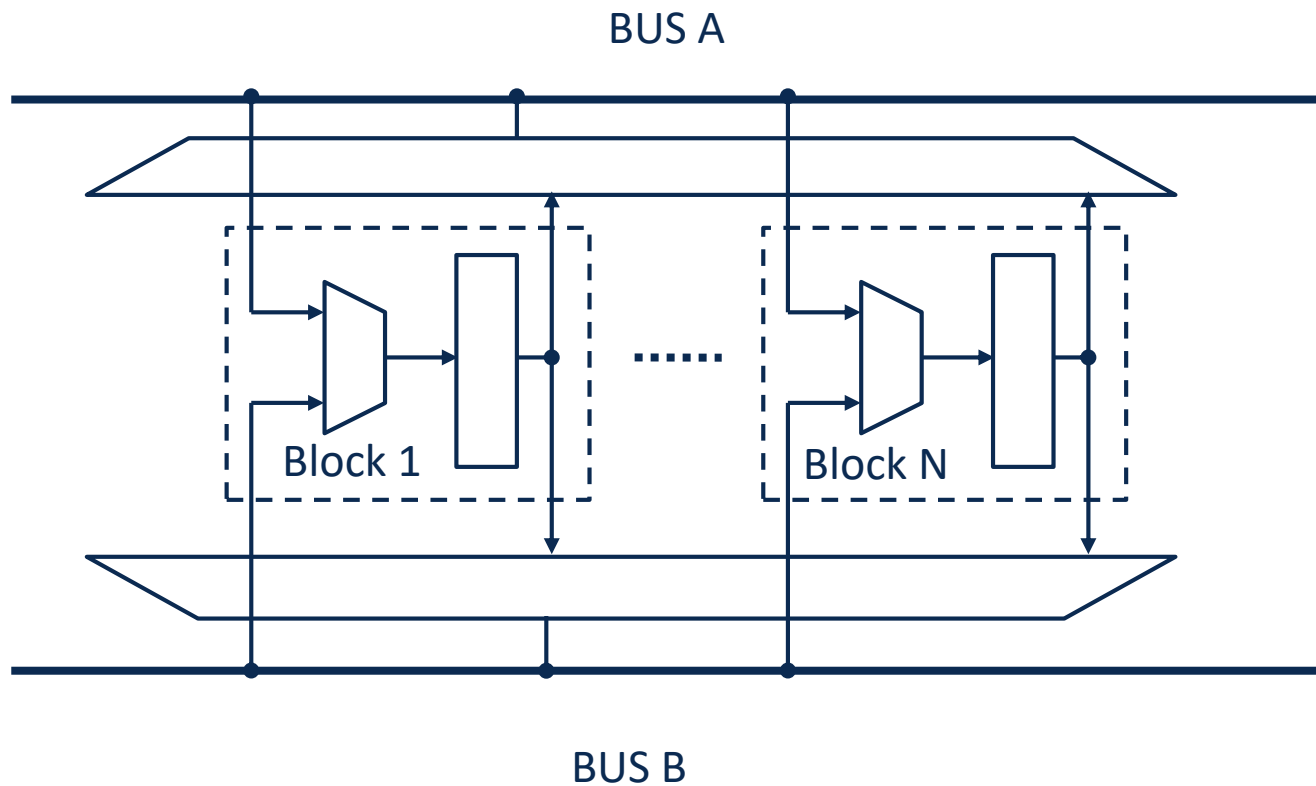
- Selecting the data sources for bus using multiplexer
- Selecting bus for the input of data path element using multiplexer
- Multiplexer Select signals are set using control unit




- Advantage: No Tri-State driver
- Number of multiplexer inputs depends on necessary data connections
- Goal: Minimization of the necessary multiplexer inputs
- Possibility of hierarchical implementation of multiplexers
- Bus Multiplexer: Selecting data source for the bus
- Input Multiplexer: Selecting data source for the input of data path element


- Example:  $C=(A+B)+A/2$

State	Data source	Number of buses
LOAD A	IN → REGA	1
LOAD B	IN → REGB	1
COMP1	REGA → ALU(OPA) REGB → ALU(OPB) REGA → SHIFT	2
COMP2	ALU(RES) → ALU(OPA) SHIFT → ALU(OPB)	2
STORE	ALU(RES) → OUT	1

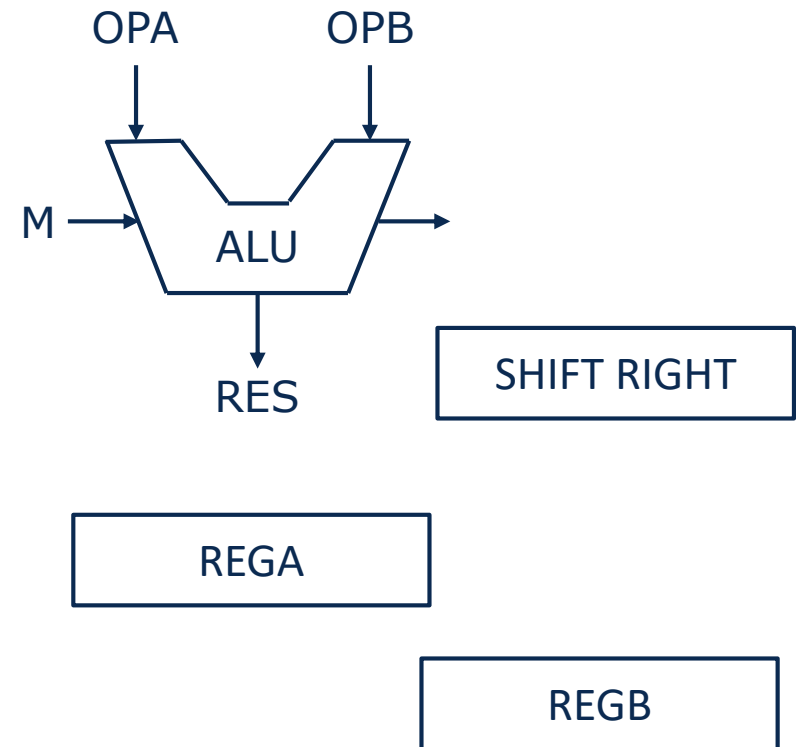


- → 2 Data buses needed (BUS A, BUS B)

 

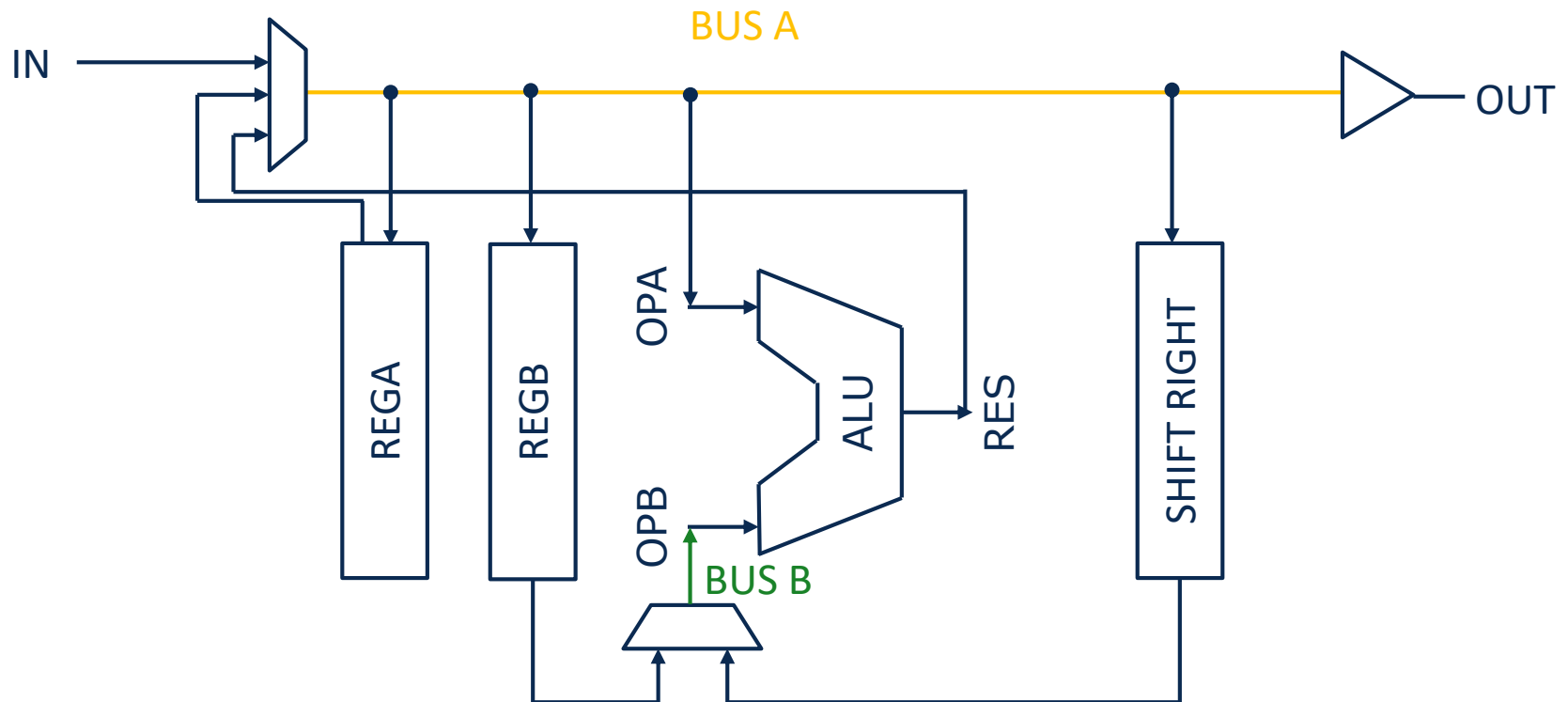


- Reduction of Multiplexer

 





- The previous bus systems require **application-specific** control by a control unit
- They are not standardized → Integrating prefabricated building blocks (IP) is difficult.
- Complex digital systems require flexible, standardized bus systems
- Basic concept:
  - Standardized bus interface (**Data, Address, Control and Status signals**)
  - Addressing Bus users (ID)
  - Access via ports (similar to Memory)
  - Internal bus control logic is responsible for data transfer and monitoring the access

 

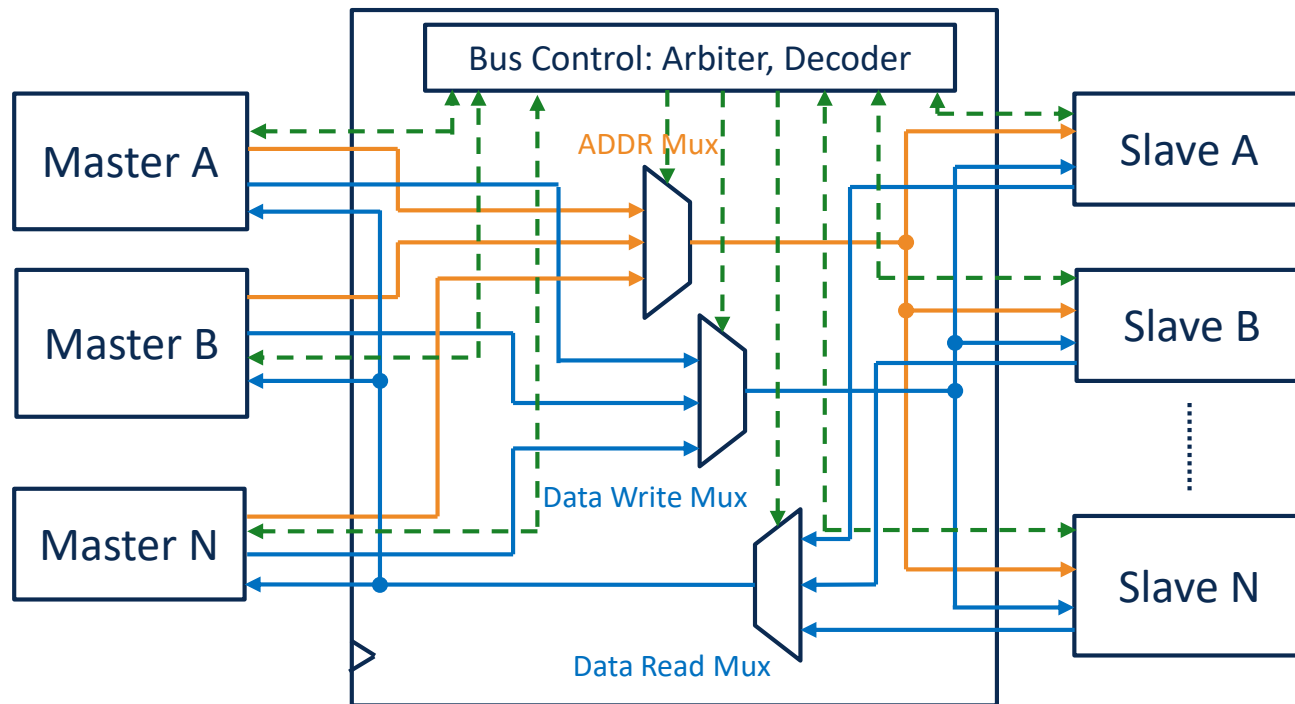- „Circuit Switched Network“ → Multiplexer Bus
- Master and Slave components with standardized bus interface
- Arbitration and Prioritization of access by Bus Controller
- Synchronous (CLK)
- Sequential access (Address cycle, Data cycle, Wait cycles when Bus „busy“, Burst)
- Examples: ARM AHB, WishBone, ...




 - Advantages:
  - Standardized bus interface
  - Low latency (few clock cycles)
  - Easy to implement (synchronous design)
- Disadvantages:
  - Local synchronous clocking for "global wiring" on the chip
  - Higher costs regarding chip area and power consumption
  - can limit the maximum clock frequency
- Example: Music 2 SIMD Cluster





Infineon/IMC MuSiC2 SIMD  
Cluster (conv. interconnect)

 - „Packet Switched Network“ → Routing of Packets through the network (**Router**)
- Flexible topologies possible
- Standardized package format and components interface
- High performance (data throughput, latency) in complex systems through parallelism
- Global asynchronous realization possible, individual cycles of the individual components




 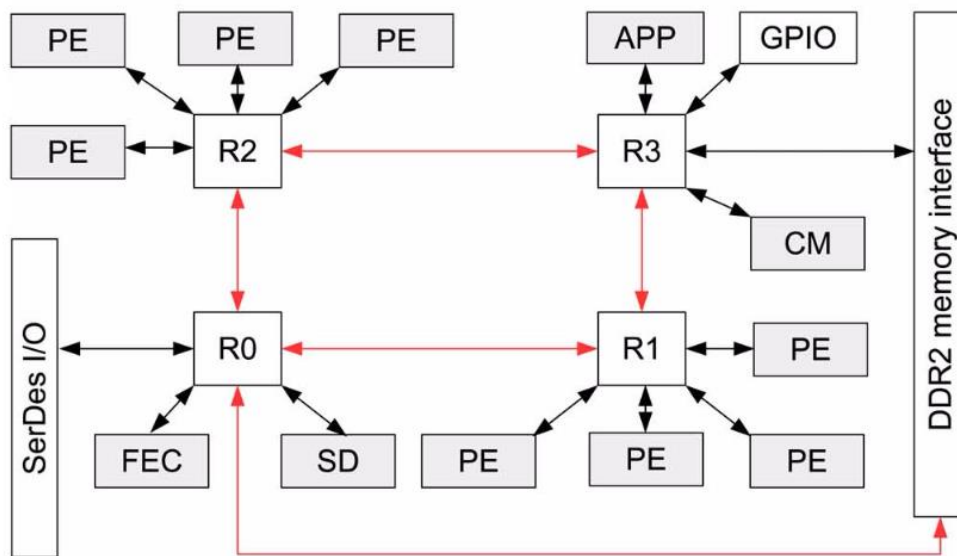- Tomahawk2: Software-Defined Radio baseband processor, developed by TUD-MNS and TUD-HPSN
- Connecting system components in a NoC
- Point-to-point connections with fast serial links → compact layout



Höppner, Sebastian and Walter, Dennis and Hocker, Thomas and Henker, Stephan and Hänzsche, Stefan and Sausner, Daniel and Ellguth, Georg and Schlüssler, Jens-Uwe and Eisenreich, Holger and Schüffny, René, An Energy Efficient Multi-Gbit/s NoC Transceiver Architecture With Combined AC/DC Drivers and Stoppable Clocking in 65 nm and 28 nm CMOS, IEEE Journal of Solid State Circuits 50 (2015), no. 3, 749-762,

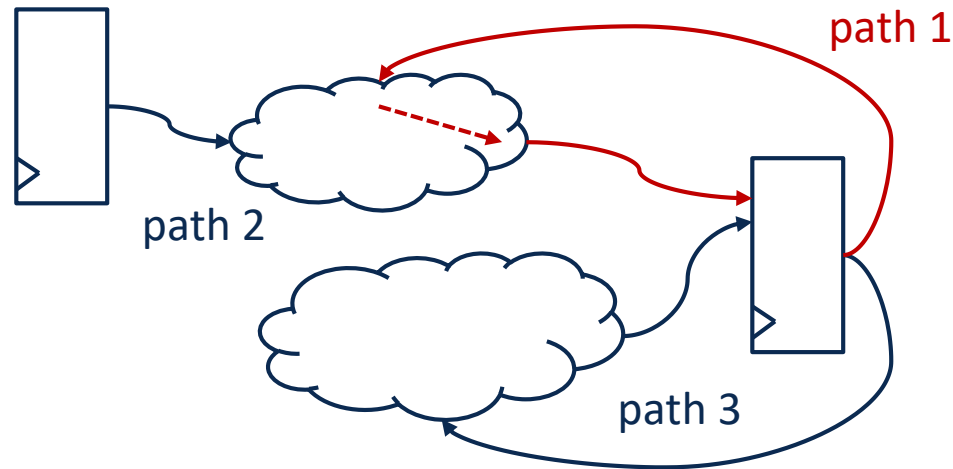- Clock frequency and Data throughput, measured in
  - [GHz]
  - Operations per seconds [GOPS]
- Chip area, measured in
  - [ $\mu\text{m}^2$ ]
  - NAND2 equivalents (technology-independent standardization)
- Energy per calculation step, measured in
  - [pJ]




- Data paths have many timing paths with delay  $t_{\text{delay}}$ 
  - Starting point: register output
  - End point: register input
  - Clock frequency is limited by the **critical path** ( $f_{\text{max}} \approx 1/\max(t_{\text{delay}})$ )
- Only few data path elements are critical to timing



- $f_{\max} = 1/\max(t_{\text{delay}}) \rightarrow 285\text{MHz}$
- Latency: 4 clock cycles
- Data throughput:  $285\text{MHz}/4 = \mathbf{71\text{ MOP/s}}$  (without Pipelining)




- Logic Re-Timing:

 



- $f_{\max} = 1/\max(t_{\text{delay}}) \rightarrow 333\text{MHz}$
- Latency: 4 clock cycles
- Data throughput:  $333\text{MHz}/4 = \mathbf{83\text{ MOP/s}}$  (without Pipelining)
- Can be done automatically by synthesis tools

- Inserting register stages:

 


- $f_{\max} = 1/\max(t_{\text{delay}}) \rightarrow 500\text{MHz}$
- Latency: 5 clock cycles
- Data throughput:  $500\text{MHz}/5 = \mathbf{100\text{ MOP/s}}$  (without Pipelining)
- Arithmetic Circuit IP (RTL) often configurable in terms of number of clock cycles needed (e.g., Synopsys Design Ware)

 
 
- Implementation of sequential processes
- Register values in time step  $i$  are the basis for calculation in step  $i+1$
- Advantages:
  - Shorter logic delay time (calculation in several clock cycles)
  - Low hardware costs (reuse of blocks in different clock cycles)
- Disadvantages:
  - Longer calculation time



 
- Latency  $N$  clock cycles
- Data rate  $1/N$  operations per cycle



  
- **Parallel** processing of subtasks (pipelining), by:
  - Splitting the logic per computing step into **separate** circuits ("Loop Unrolling")
  - Or: inserting register stages into combinational arithmetic blocks



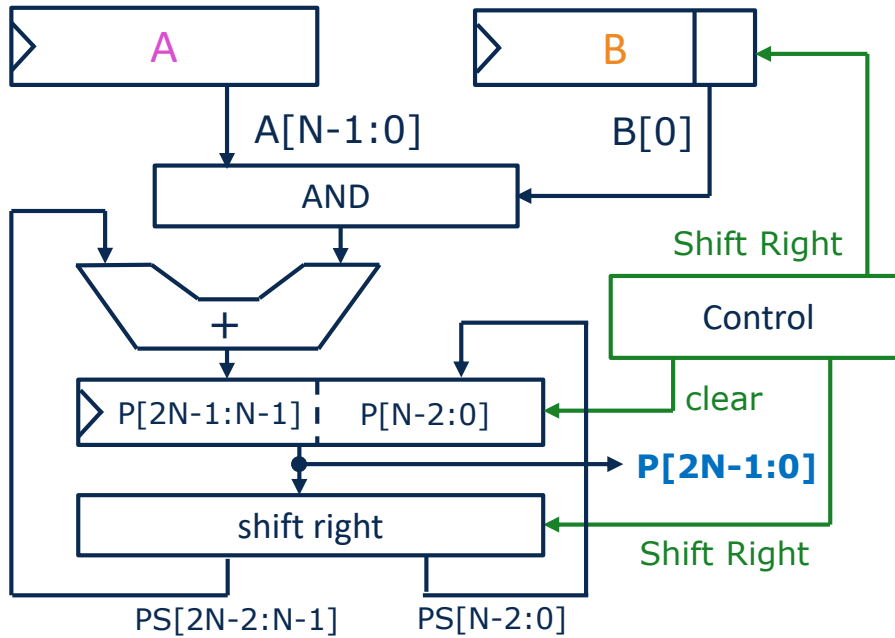- Latency  $N$  clock cycles
- Data rate 1 operation per clock cycle




				1	0	0	1	
				1	0	0	1	1
+				0	0	0	0	0
+			1	0	0	1		1
+		0	0	0	0	0		0
<b>P</b>	0	0	1	0	1	1	0	1

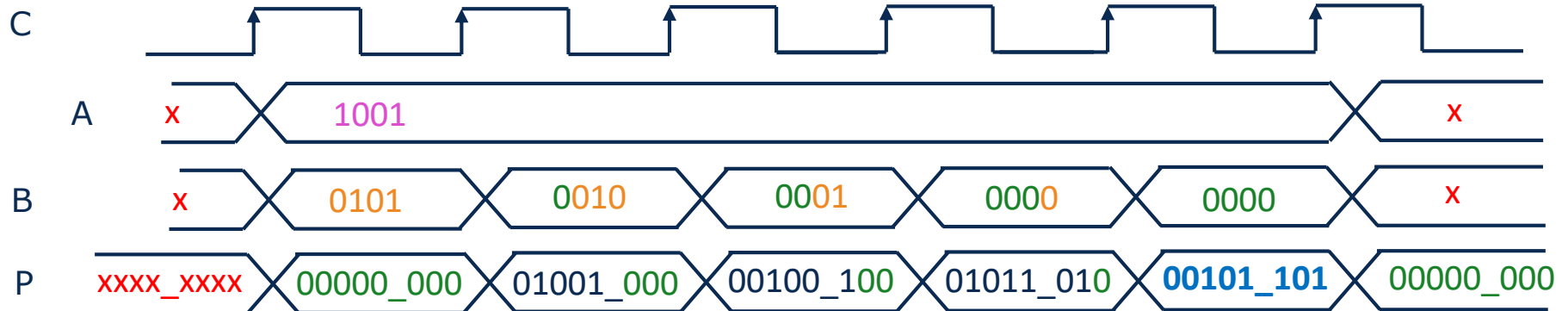

→ Output in  $N+1$  clock cycles

 - Inserting register stages in a binary multiplier
- Latency: 4 clock cycles, Data throughput: 1 output/cycle



- We discussed:
  - Data path building blocks
  - Memory architectures
  - Bus systems
- Timing optimization for sequential data path blocks
  - Inserting register stages
  - Sequential Re-Timing
  - Pipelining


# Hardware Implementation of Algorithms



- Algorithms can be described as:
  - Text
  - Equations
  - (Pseudo-) Code
  - ...
- Scenario 1:
  - Programming a given hardware (**Processor**)
    - Given data path, memory architecture, instruction set
  - **Mapping** the code to the hardware using a compiler
- Scenario 2:
  - Design of Algorithm Specific Hardware (ASIC)
  - **Design** of data path, memory architecture, control flow

- Formal representation of data flow:

 - Operations  $V = \{v_0, v_1, v_2, \dots\}$
- Delay  $D = \{d_0, d_1, d_2, \dots\}$
- Set of edges  $E = \{e_{ij}, \dots\}$
- $\text{Pred}_{v_i}$  all predecessors of  $v_i$
- $\text{Succ}_{v_i}$  all successors of  $v_i$





- The "runtime" of an operation is specified in **clock cycles**
- Presenting **start time** and **delay time**
- Specifying the necessary **hardware resources**

- Determines the schedule of operations
- Consideration of constraints
  - runtime (Timing Constraints)
  - Hardware complexity (Resource Constraints)
- Scheduling is an optimization problem
  - Sets the start time of operations
  - Follows the given boundary conditions
  
- Result of scheduling:
  - Creating a DFG
  - Derived from this:
    - Data path
      - Which and how many data path blocks?
      - Which and how many registers?
      - How many buses?
    - Register transfer after designing the control unit

- Numerical DGL solution:  $y'' + 3xy' + 3y = 0$
- Forward Euler method
- Saving output in RAM to ADDR

 
```
WHILE (x<a) DO
  x1:=x+dx;
  u1:=u-(3·x·u·dx)-(3·y·dx);
  y1:=y+(u·dx);
  x := x1; u := u1; y :=y1;
  addr := addr+1; STORE(y1,addr);
ENDWHILE
```



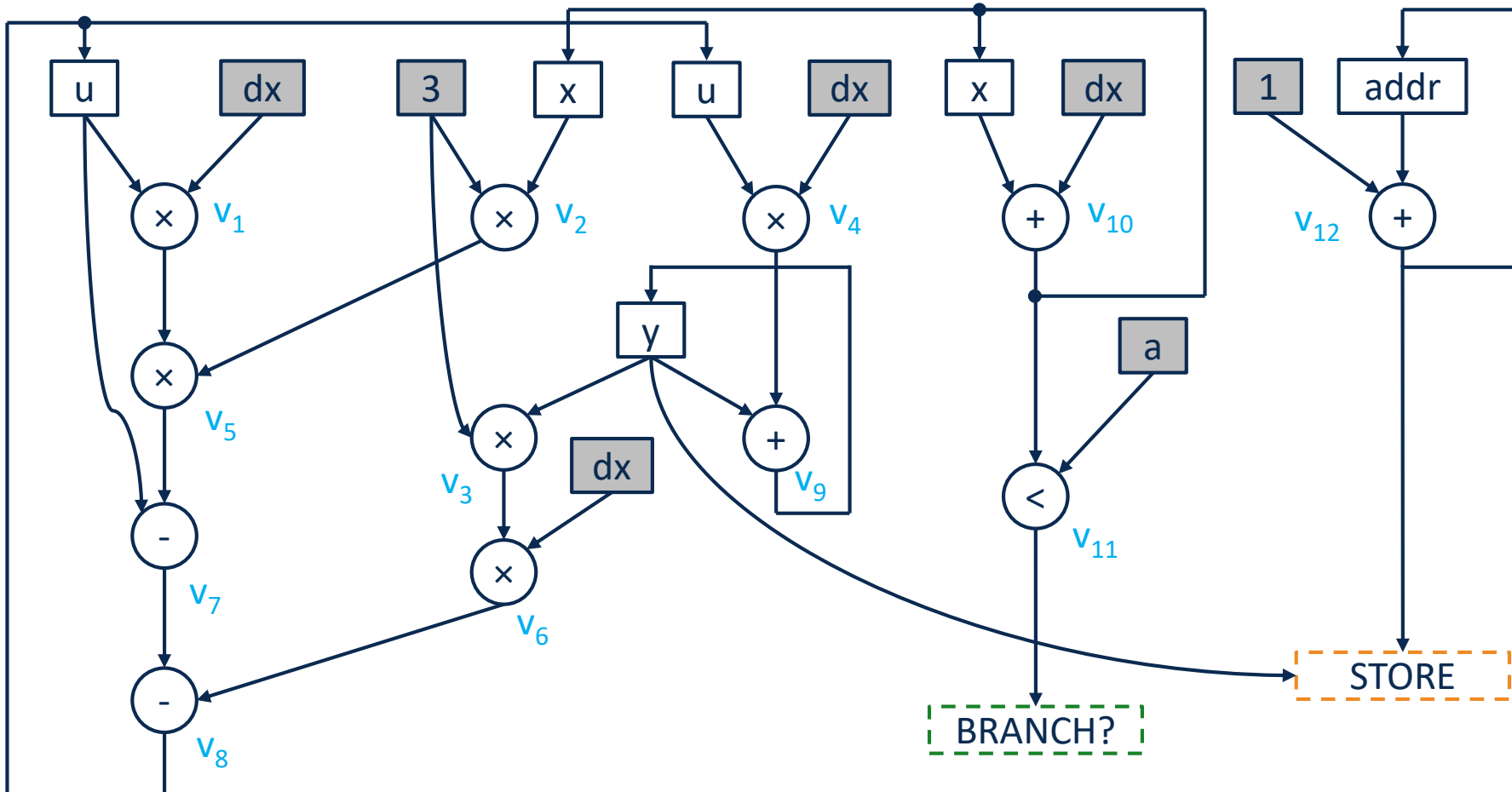


Source: Scheduling Algorithms for High-Level Synthesis, Zoltan Baruch

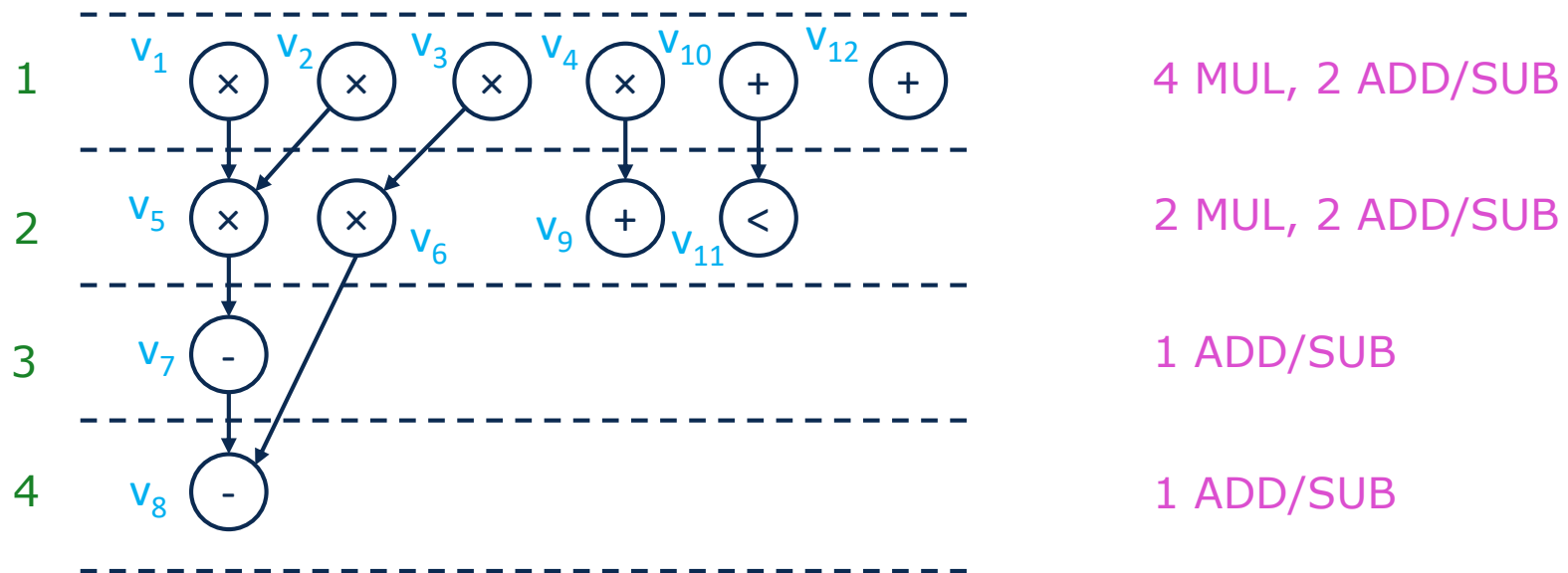- Scheduling Algorithm:
  - Repeat for all nodes  $v_i$
  - Select a  $v_i$  whose **predecessors** are all assigned
    - Terminate  $v_i \rightarrow t_i = \max(t_j + d_j)$  for all  $j$  from  $\text{Pred}_{v_i}$  ( $\rightarrow$  earliest time)
  - Until all  $v_i$  are assigned



 
**$\rightarrow$  4 MUL, 2 ADD/SUB**

- Scheduling Algorithm :
  - Repeat for all nodes  $v_i$
  - Select a  $v_i$  whose **successors** are all assigned
    - Terminate  $v_i \rightarrow t_i = \min(t_j - d_j)$  for all  $j$  from  $\text{Succ}_{v_i}$  ( $\rightarrow$  latest time)
  - Until all  $v_i$  are assigned




$\rightarrow$  2 MUL, 4 ADD/SUB

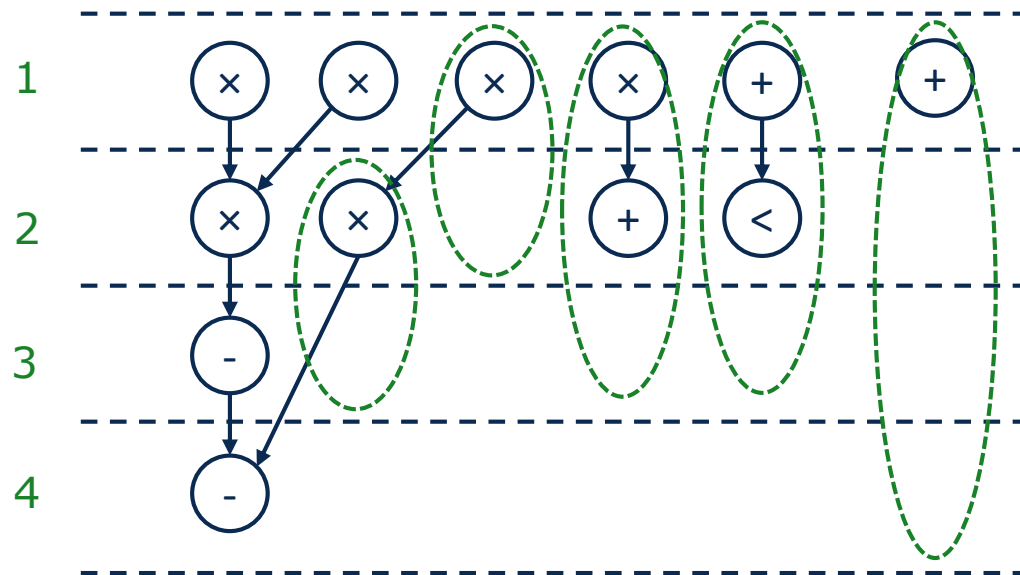- Degree of freedom of start time of operations without affecting the latency of DFG






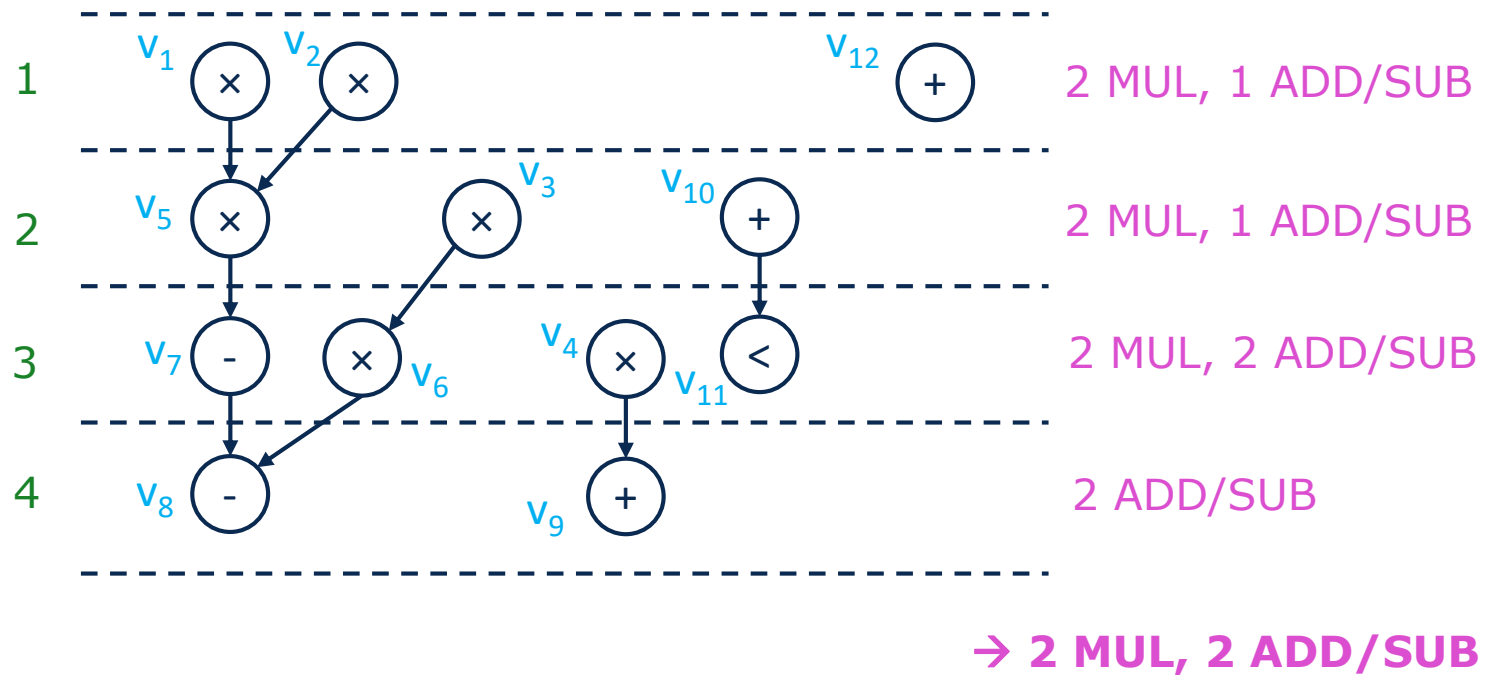
- Scheduling for
  - given hardware resources (chip area)
  - Extreme case: minimal hardware (modules, buses)
  - Use of mobility (no increase in latency):



 
- Inserting additional clock cycles → Increasing the latency



 
- Scheduling for a given processing time
- Application e.g. digital signal processors (DSP) with real-time requirement → Output must be available according to the given number of cycles
- Example: Minimal Hardware with latency = 6 clock cycles



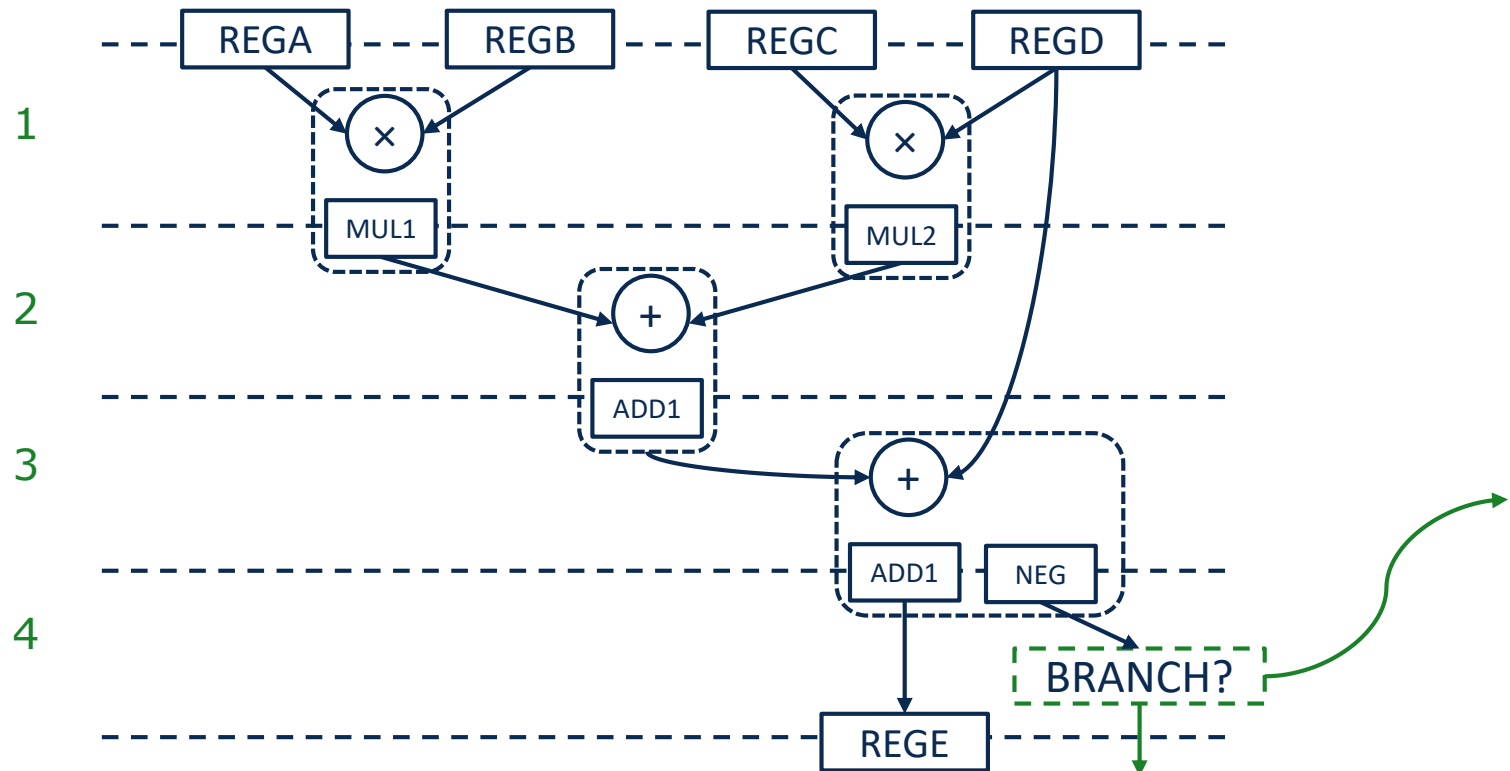
- Detailed DFG with explicit representation of registers
- Visualization of data storage → **Hardware register**
  - Basic for designing pipelines
  - Explicit representation of **branches**



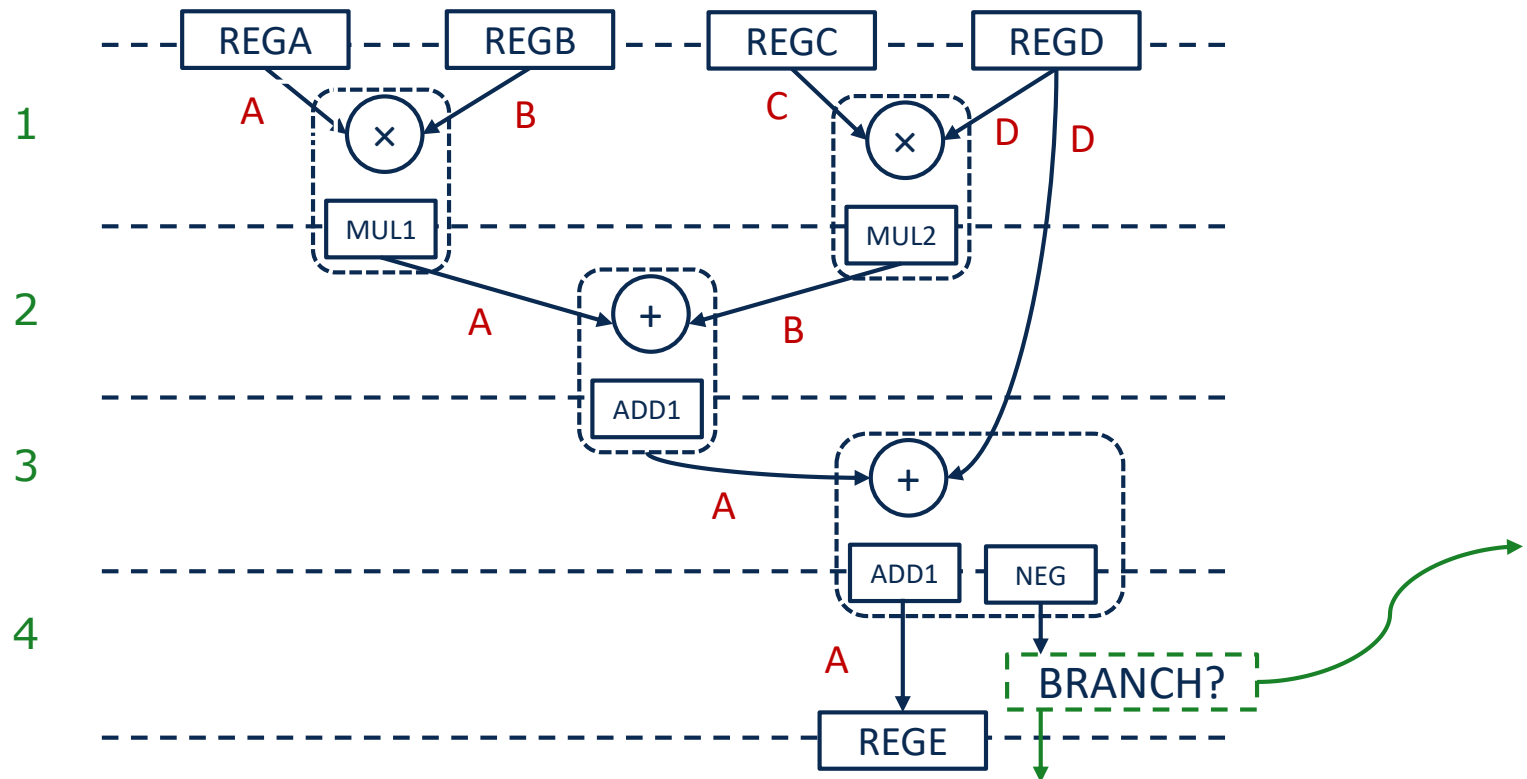
- Assigning **data buses** to edges of the DFG
- → Determines the number of necessary data buses



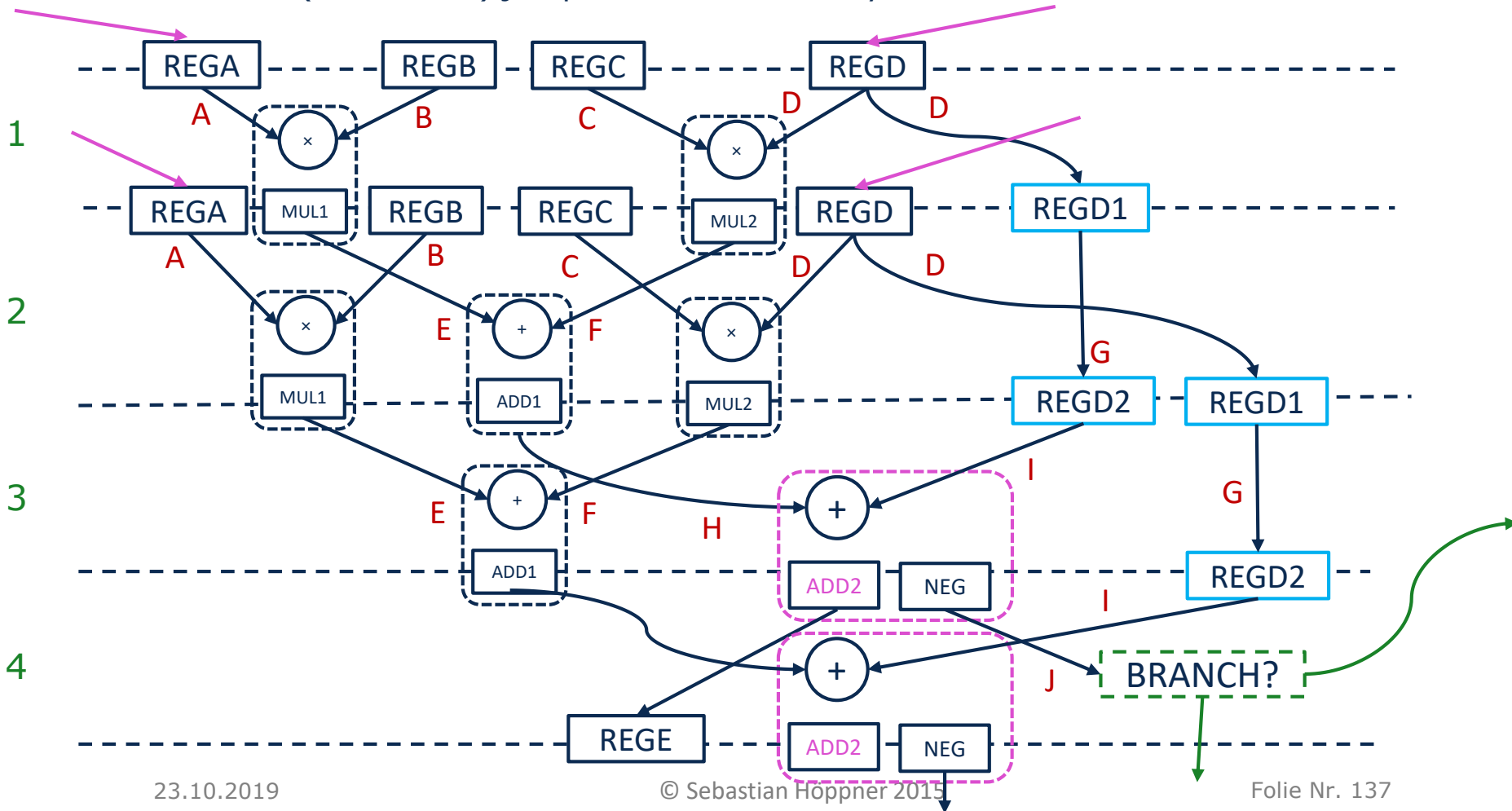- Building pipelines by adding (if needed):
- Registers, Data path blocks, Buses
- Throughput of 1 output per clock cycle at N clock latency
- Be aware of (conditional) jumps! → → if necessary discard results




- Sequential SRAM access

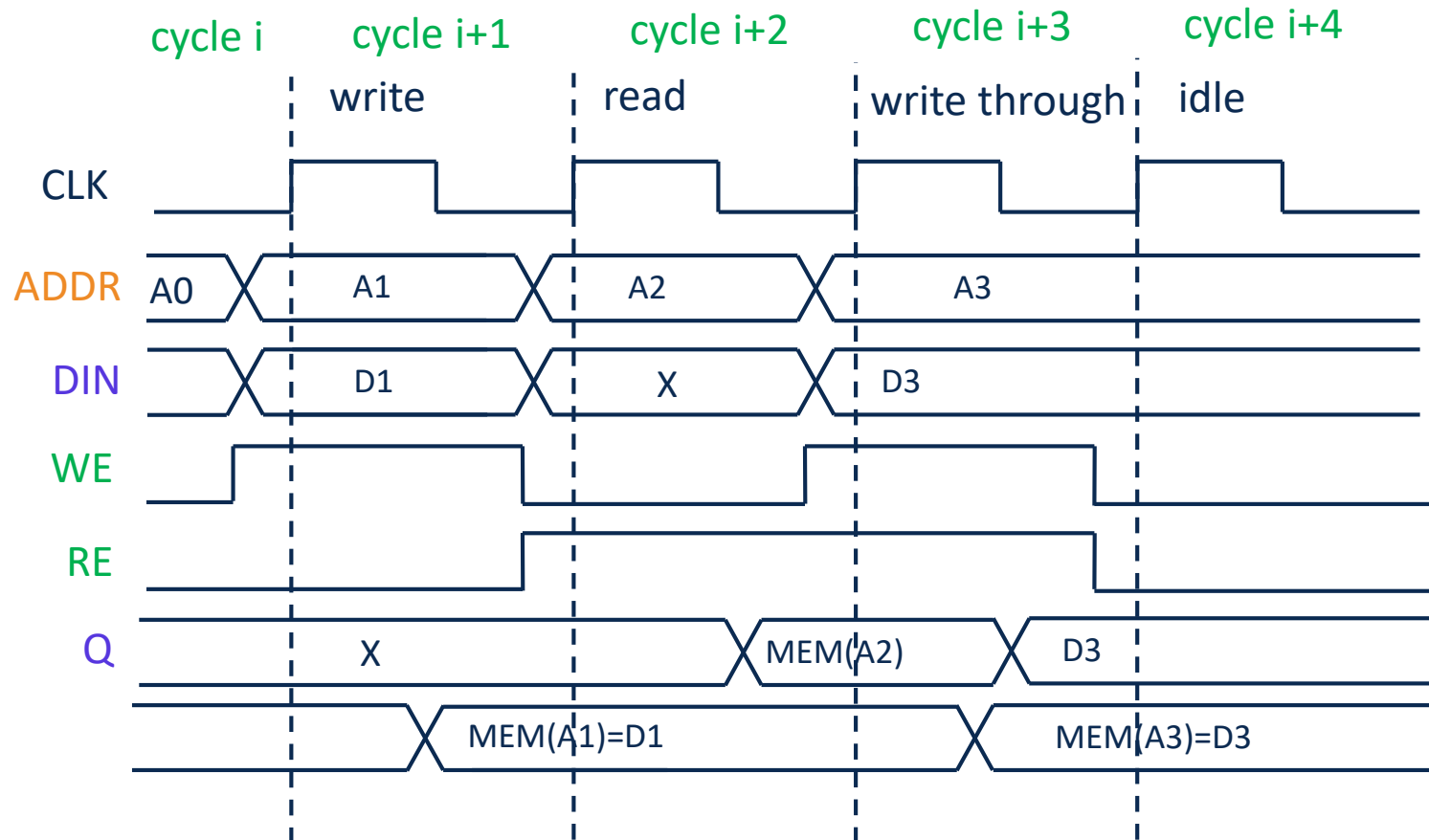

- Calculate the address through Fixed-Point ALU
- Consider **SRAM signals** such as registers
- Example:


Address	Action
0	Read to REGA
1	Read to REGB
2	Read to REGC

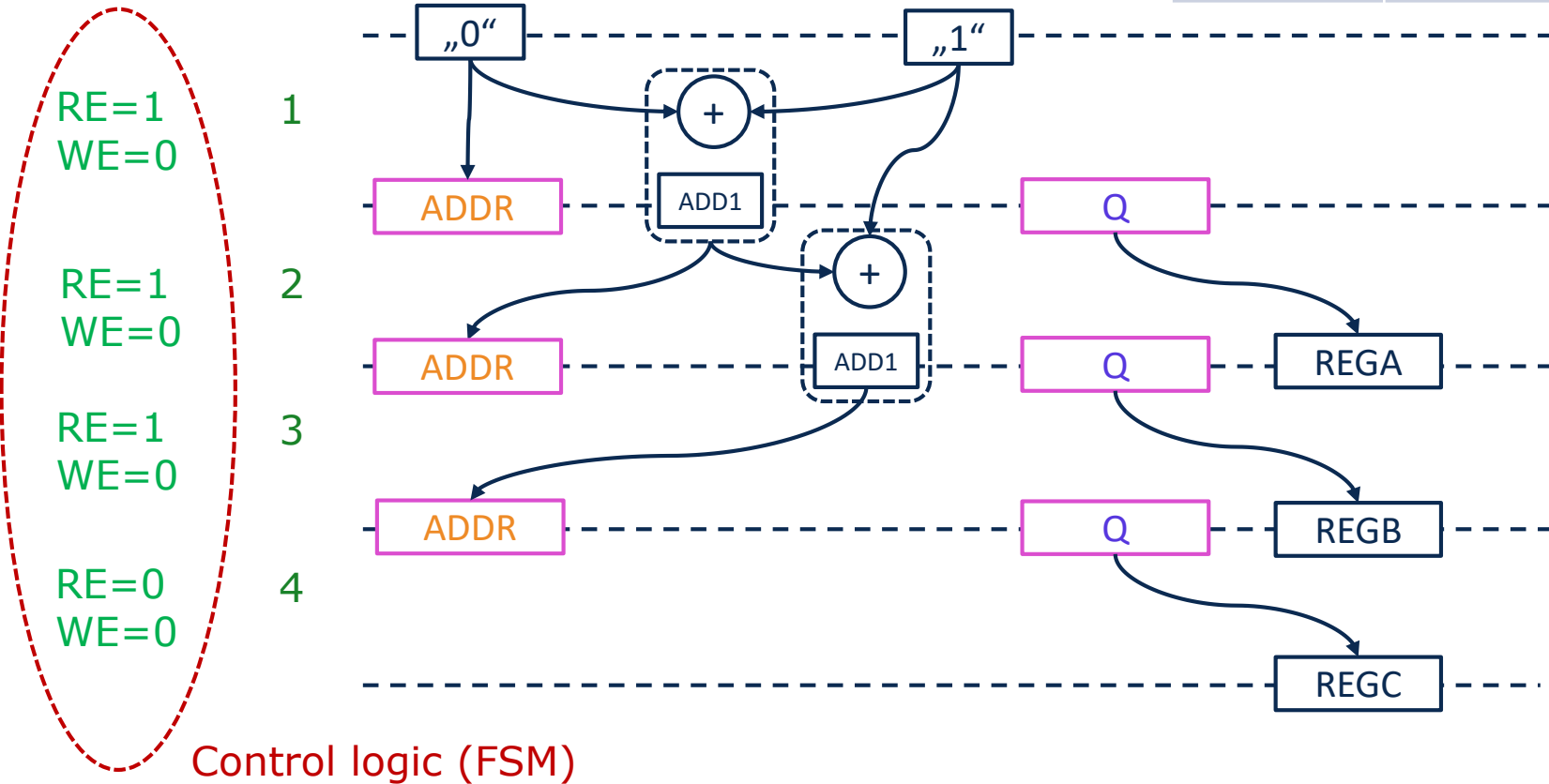




- Calculate the address through Fixed-Point ALU
- Consider **SRAM signals** such as registers
- Example:

Address	Action
3	Write from REGD
4	Write from REGE
5	Write from REGF

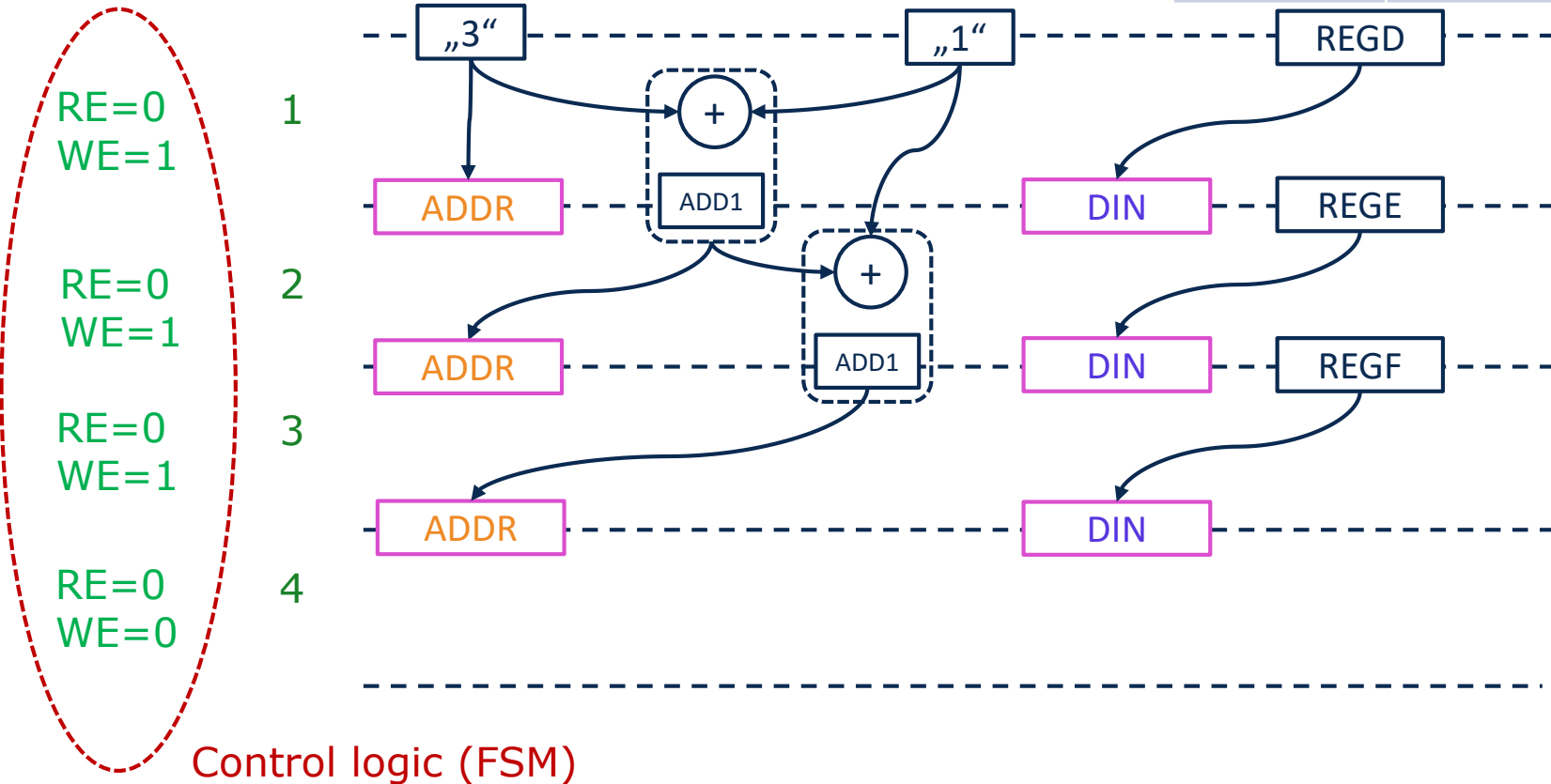


- Constructing data path from a DFG
- Determine the number of
  - Modules
  - Registers
  - Buses/ data connections
- Design of data path with bus system (for example multiplexer) → see section [Data paths / Buses](#)


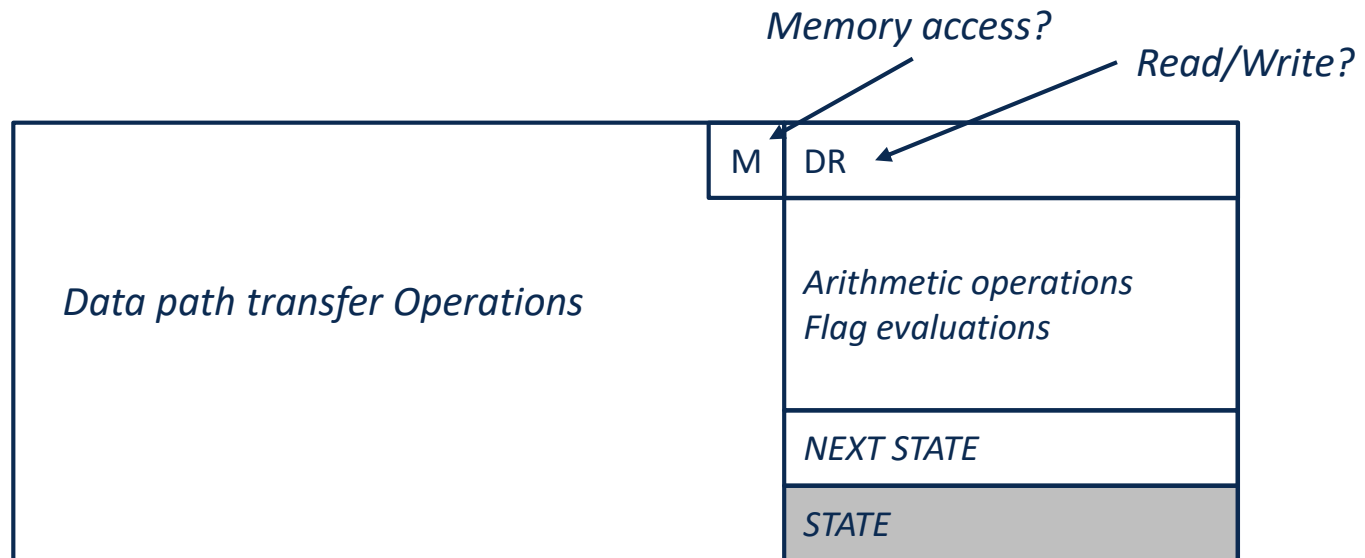
- Representation of processes in Register Transfer Notation



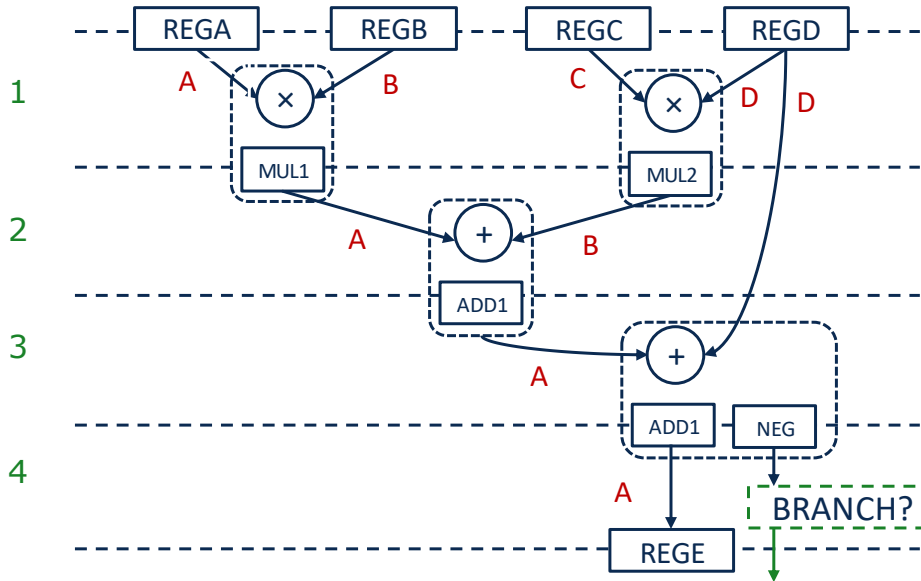- A register transfer block describes **one** clock cycle




A: REGA → MUL1, OPA B: REGB → MUL1, OPB C: REGC → MUL2, OPA D: REGD → MUL2, OPB	S_2 S_1
A: MUL1, R → ALU1, OPA B: MUL2, R → ALU1, OPB	ALU1: ADD S_3 S_2
A: ALU1, R → ALU1, OPA D: REGD → ALU1, OPB	ALU1: ADD S_4 S_3
A: ALU1, R → REGE	ALU1, NEG? 0: S_5 1: S_6 S_4

  

- RT representation defines the states and state transitions of FSM
- Conditions: Flags
- RT representation defines the signals → output logic of FSM
- Switching buses (tristate driver, multiplexer)
  - Configuring data path blocks (ADD / SUB)...
- → see section FSM

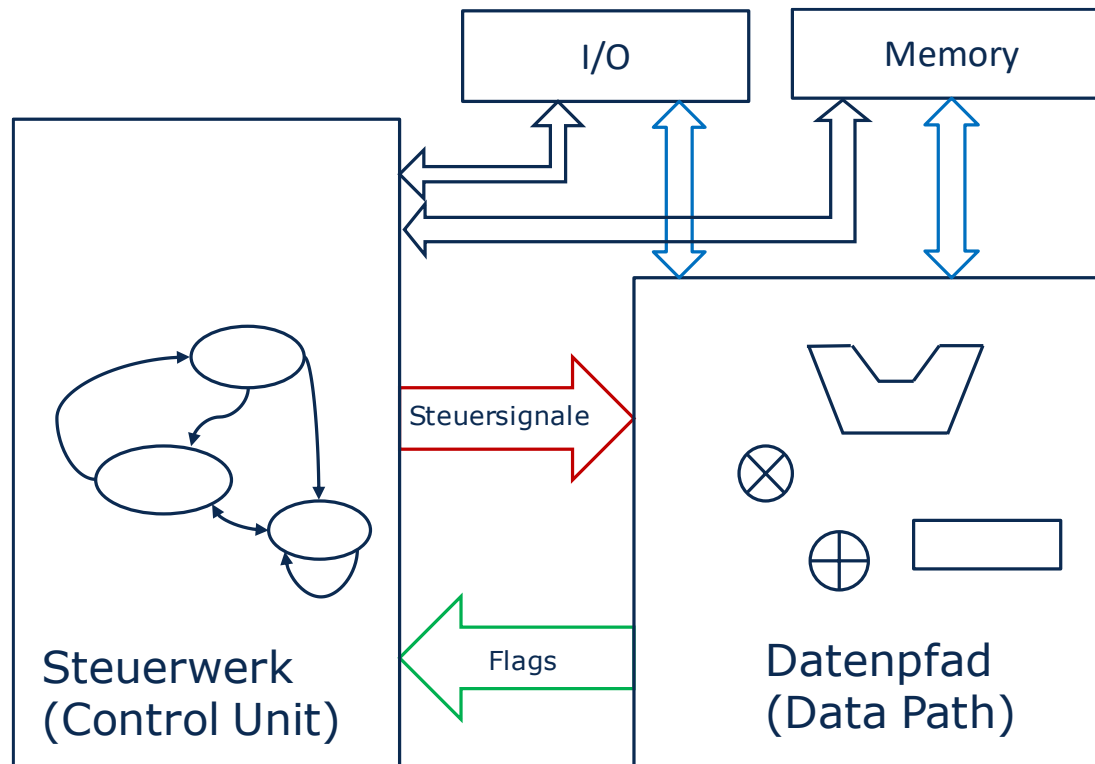
- Presentation of the data flow graph, scheduling and optimization
- ASAP, ALAP, Resource Constraints and Timing Constraints
  - Pipelining
- Register Transfer Sequence → Derive data path and FSM



- Neuromorphic hardware for the Human Brain Project
  - Brain simulation
  - Technical applications, e.g. robotics
  - Challenges:
    - Simulation of a **large number** of neurons and synapses in **biological real time**
- Development of a many-core computer with > 4 million ARM processors (SpiNNaker 2)
  - Architecture Development → University of Manchester
  - Chip Design → TU Dresden




Human Brain Project

 

<http://bluebrain.epfl.ch>





Source: Human Brain Project

 




SpiNNaker 1 Chip

  - Calculation of dynamics of neurons and synapses
- Often used:  $e^x$
- Number format: 32-bit, s16.15 fixed-point
- Processor Core (ARM Cortex M4)
  - So far **exp()** realized in software ( $\approx 30$  clocks)
  - $\rightarrow$  hardware accelerator for **exp ()**,
  - Connection as AHB slave to processor






   - Dividing the argument of the function
- $e^x = e^{(x_{int} + x_{frac} + x_{lsb})}$
- Look-up tables for **integer part (int)** and **fractional part (frac)**
- 4th degree polynomial approximation for **LSBs**
- Accuracy < 1LSB for 32-bit, s16.15 fixed-point number format




 - Pipeline with 4 stages
- FIFO at output (32 values)
- Implementation in 28nm CMOS
- >500MHz clock frequency possible



Measure	exp accelerator	software exp
Throughput @500MHz	250Mexp/s	5.3Mexp/s
Time per exp, pipelined	2clks/exp	95clks/exp
Latency	6clks/exp	95clks/exp
Energy per exp (nominal)	0.44nJ/exp	25nJ/exp
Energy per exp (0.7V/154MHz)	0.21nJ/exp	12nJ/exp
Total area	10800 $\mu\text{m}^2$	-

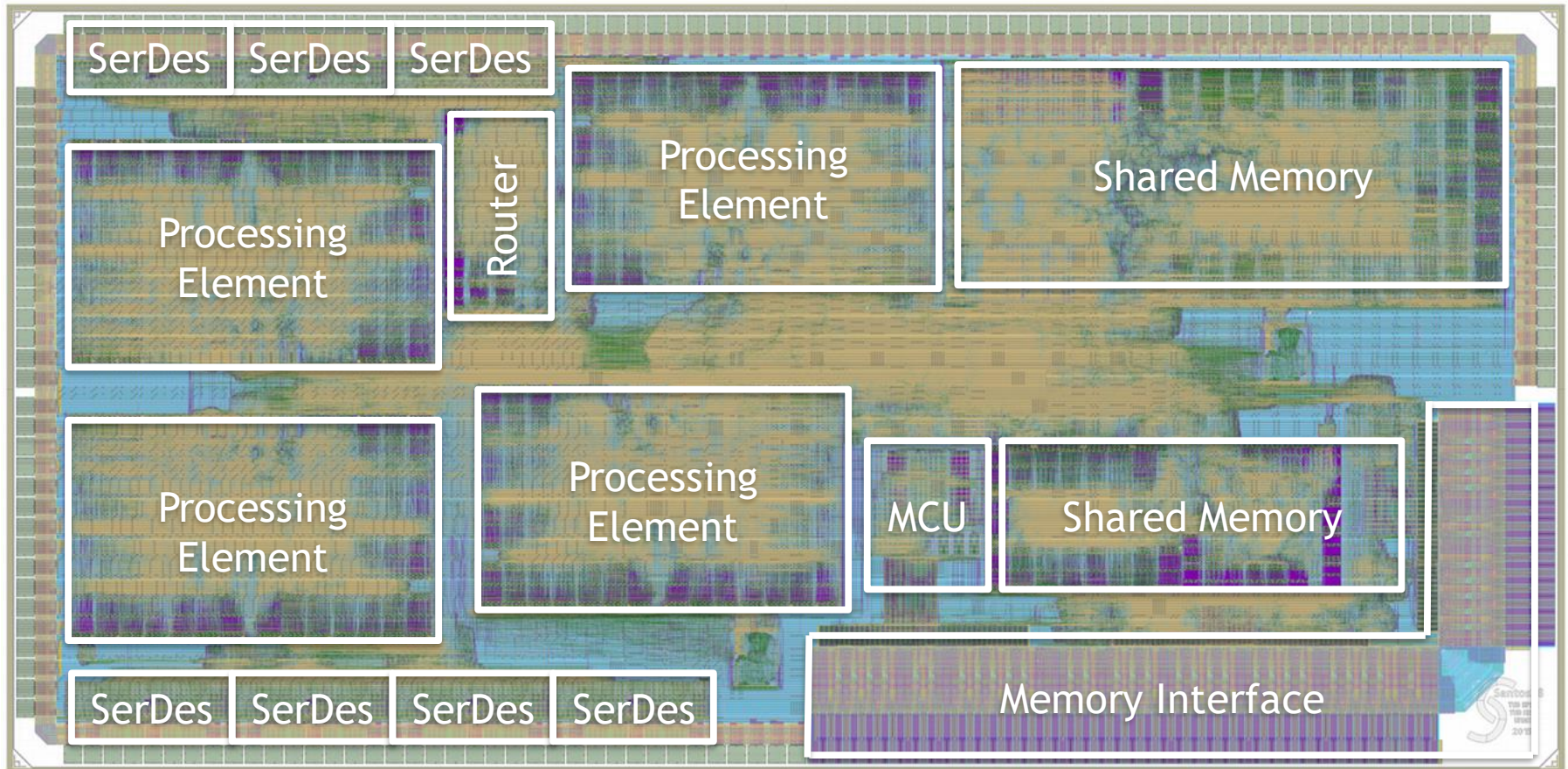J. Partzsch et al., "A fixed point exponential function accelerator for a neuromorphic many-core system,"  
 2017 IEEE International Symposium on Circuits and Systems (ISCAS), Baltimore, MD, 2017, pp. 1-4.  
 doi: 10.1109/ISCAS.2017.8050528




- Test chip: Santos
- 28nm SLP CMOS, 18mm<sup>2</sup>
- Component test chip for Neuromorphic Supercomputer
- 4 processing elements, memory interface, fast serial I/Os



## Modul Neuromorphic VLSI-Systems

Neuromorphe Systeme

Analoger CMOS-Schaltungsentwurf

 

- Grundlagen zu neuronalen Netzen und ihrer technischen Realisierung
- Integrierte analoge Schaltungen: Entwurf, Simulation, Verifikation
- Praktischer Schaltungsentwurf und Layout mit Cadence



Human Brain Project